

ECE 341

Introduction to Computer Hardware

Instructor: Zeshan Chishti
zeshan@pdx.edu

Fall 2014

Portland State University

When and Where?

- When: Mondays and Wednesdays 4:40 - 6:30 PM
- Where: EB 103
- Office hours: Mondays and Wednesdays after class, or by appointment
- Webpage: <http://ece.pdx.edu/~zeshan/ece341.htm>
- TA: Leela Kamalesh Yadlapalli
- TA office hours: TBA
- Go to the course webpage for:
 - Class slides
 - Course syllabus and schedule
 - Grading policies
 - Homework assignments and solutions

Course Information

- Textbook: Computer Organization and Embedded Systems, 6th Edition, *Hamacher, Vranesic, Zaky and Manjikian*. McGraw-Hill, 2011. ISBN 9780073380650 / 0073380652
- Expected background: CS201 or equivalent
 - Basic knowledge of computer organization
 - Data representation in binary, decimal, and hexadecimal notation
 - Basic knowledge of instruction set architecture
 - Assembly language programming

Grading Policy

- Homeworks 35%
 - 8 homework assignments, top 7 chosen for each student to contribute towards the 35%
- Midterm Exam 25%
- Final Exam 40%
- Grading scale (tentative):
 - A: 92-100% A-: 87-91.5%
 - B+: 83-86.5% B: 79-82.5% B-: 75-78.5%
 - C+: 71-74.5% C: 67-70.5% C-: 63-66.5%
 - D+: 59-62.5% D: 55-58.5% D-: 50-54.5%
 - F: Below 50%


Other Policies

- All homeworks due in class. No extensions given
- Submit homework to the instructor soon after entering the class
- You can also submit homeworks via email before the start of class
- Midterm exam in class during week 6
 - Wednesday, November 5, 4:40 – 6:30 PM
- Final exam will cover entire course with more emphasis on material taught after the midterm exam

What this course is all about?

This course is about designing a computer in hardware

 End Goal: To understand the hardware implementation of different components of a modern computer



Basic functional units of a computer

Course Topics

- Digital logic – gates, flip flops, multiplexers, state machines
- Computer arithmetic
- Basic computer architecture – data path, control, and buses
- Pipelining hardware
- CISC vs RISC architectures
- Memory hierarchy and virtual memory
- Input/output techniques – polling, interrupts, and DMA

Lecture # 1


DIGITAL LOGIC DESIGN

Lecture Topics

- Combinational Logic
 - Logic gates and logic circuits
 - Synthesis of logic functions
 - Logic expression minimization
- Reference: Appendix A of the textbook (pages 466-481), including sections A.1, A.2, A.3, and A.4, excluding A.3.1 and A.3.2


Logic Circuits

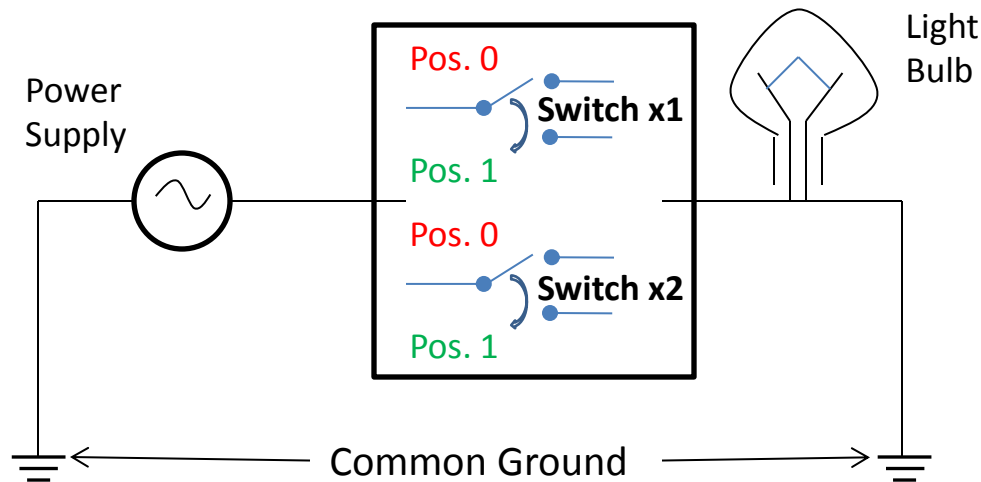- Example: Light bulb controlled by two switches



- Input: Switch positions
 - Represented as binary variables **x1** and **x2** whose values can be either 0 or 1
- Output: Condition of light bulb
 - Represented as binary variable **f** with possible values 0 (off) or 1 (on)
- Logic circuit: Interconnection of switch terminals
 - Output=1 if a closed path exists from supply to the bulb through the switch network

OR function (Parallel Connection)

 

If either x_1 or x_2 is in the 1 position, the light is on (output = 1)

x_1	x_2	$f(x_1, x_2) = x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

- OR function is represented by the “+” symbol:

$$f = x_1 + x_2$$

- Basic properties of OR operation:

$$x_1 + x_2 = x_2 + x_1$$

$$(x_1 + x_2) + x_3 = x_1 + (x_2 + x_3)$$


$$1 + x = 1$$

$$0 + x = x$$

$$x + x = x$$

- Extendible to n variables: $f = x_1 + x_2 + \dots + x_n$ is equal to 1 if any variable $x_i = 1$

AND function (Series Connection)

 

Light is on (output = 1) only if both x1 and x2 are in the “1” position

x1	x2	$f(x1, x2) = x1.x2$
0	0	0
0	1	0
1	0	0
1	1	1

- AND function is represented by the “.” symbol:

$$f = x1 . x2$$

- Basic properties of AND operation:

$$x1 . x2 = x2 . x1$$

$$(x1 . x2) . x3 = x1 . (x2 . x3)$$


$$1 . x = x$$

$$0 . x = 0$$

$$x . x = x$$

- Extendible to n variables: $f = x1.x2.....xn$ is equal to 1 if for all i, $xi = 1$

XOR function (Exclusive-OR Connection)

 

If $x1 = x2 = 0$, light is off (output = 0).
Flipping any switch flips the output

x1	x2	$f(x1, x2) = x1 \oplus x2$
0	0	0
0	1	1
1	0	1
1	1	0

- XOR function is represented by the “ \oplus ” symbol:

$$f = x1 \oplus x2$$

- Basic properties of XOR operation:

$$x1 \oplus x2 = x2 \oplus x1$$

$$(x1 \oplus x2) \oplus x3 = x1 \oplus (x2 \oplus x3)$$

$$1 \oplus x = \bar{x}$$

$$0 \oplus x = x$$

$$x \oplus x = 0$$

- Extendible to n variables: $f = x1 \oplus x2 \oplus \dots \oplus xn$ is equal to 1 if there is an odd number of input variables with values of 1, otherwise f is equal to zero

NOT function

x	f(x) = NOT(x)
0	1
1	0

NOT function complements
(inverts) its input

- NOT function is represented by the “ $\overline{}$ ” symbol

$$f = \bar{x}$$

- Important properties of NOT function:

$$\overline{\overline{x}} = x$$

$$x + \bar{x} = 1$$

$$x\bar{x} = 0$$

$$\overline{w + y} = \bar{w}\bar{y}$$


$$\overline{wy} = \bar{w} + \bar{y}$$

} De Morgan's
Law


Logic Gates

Electronic circuits that perform basic logic operations are called **logic gates**

 
Logic gates are often represented by logic symbols



OR

 

AND

 


XOR



NOT

Combinational Logic

 


- Each input combination corresponds to a unique set of output values
- Logic function governs the relationship between inputs and outputs
- Logic function is implemented by a logic network
 - A logic network is a combination of logic gates interconnected according to the logic function specification

Logic Function Representation

Three different ways to represent a logic function

(a) Logic Network

 

(c) Truth Table

x_1	x_2	$\overline{x_1}.x_2$	$x_1.\overline{x_2}$	f
0	0	0	0	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

(b) Logic Expression $f = (\overline{x_1}.x_2) + (x_1.\overline{x_2})$

Sum-of-Products Form

- Logic expressions are often shown in **sum of products** form
- For example: $f = (\overline{x_1}.x_2) + (x_1.\overline{x_2})$
- To simplify appearance, parentheses and “.” signs are removed, for example, $f = \overline{x_1}x_2 + x_1\overline{x_2}$
 - Each product terms represents an AND operation
 - Each addition represents an OR operation
 - Operations performed in the following order: NOT, AND, OR
- Sum of products form makes it easier to derive the logic network
 - For each product term, connect input variables to AND gate, use NOT gates wherever input needs to be inverted
 - Connect AND gate outputs to OR gate

Logic Function Synthesis

- A truth table is often used to specify a logic function
- Sum-of-products form can be derived from truth table
- Example:

x1	x2	x3	f1
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1



Required: Logic function for f1 in sum-of-products form

Steps:

1. Identify rows in the table for which $f1 = 1$
2. For each such row, write down a product term (AND) which includes all the input variables. NOT operator is applied to variables whose values are 0 in that row
3. Add the “+” operators (OR) between the product terms:

Result:

$$f1 = \overline{x1}.\overline{x2}.\overline{x3} + \overline{x1}.\overline{x2}.x3 + \overline{x1}.x2.x3 + x1.x2.x3$$

Practice Exercise # 1

- Derive the logic equation in sum-of-products form and draw the logic network for output f2 in the following truth table:

x1	x2	x3	f2
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Practice Exercise # 1

- Derive the logic equation in sum-of-products form and draw the logic network for output f2 in the following truth table:

x1	x2	x3	f2
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$f2 = \overline{x1} \overline{x2} \overline{x3} + \overline{x1} x2 \overline{x3} + x1 \overline{x2} \overline{x3} + x1 \overline{x2} x3 + x1 x2 \overline{x3}$$

Logic Function Equivalence

- Two logic functions are **equivalent** if they yield same outputs for each combination of inputs
- Equivalence can be determined by comparing truth tables
- Example: Compare $f1 = \overline{x1}.\overline{x2}.\overline{x3} + \overline{x1}.\overline{x2}.x3 + \overline{x1}.x2.x3 + x1.x2.x3$ with $f3 = \overline{x1}.\overline{x2} + x2.x3$

x1	x2	x3	f1
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

x1	x2	x3	$\overline{x1}.\overline{x2}$	$x2.x3$	f3
0	0	0	1	0	1
0	0	1	1	0	1
0	1	0	0	0	0
0	1	1	0	1	1
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	1	1

Equivalent

Logic Expression Minimization

- Many equivalent logic functions exist for a particular truth table
- The cost of a logic function can be measured in terms of gate count
- The objective of minimization is to reduce the implementation cost
- An expression is *minimal* if there is *no* other equivalent expression of lower cost
- Minimization is performed as a series of algebraic manipulations
- Refer to properties summarized in Table A-4
- Most important rule used in minimization is **distributive rule**:

$$w(y + z) = wy + wz$$

Logic Expression Minimization

Example: Find the minimal logic expression for

$$f1 = \overline{x1}.\overline{x2}.\overline{x3} + \overline{x1}.\overline{x2}.x3 + \overline{x1}.x2.x3 + x1.x2.x3$$

Procedure:

- Group product terms in pairs that differ only in that some variable appears complemented in one term and true in the other.
- Apply the distributive rule to factor out common subproduct terms from each group
- Apply other logic identities from Table A.4, whichever applicable

$$\begin{aligned} f1 &= \overline{x1}.\overline{x2}(\overline{x3} + x3) + x2.x3(\overline{x1} + x1) \\ &= \overline{x1}.\overline{x2}.1 + x2.x3.1 \\ &= \overline{x1}.\overline{x2} + x2.x3 \end{aligned}$$

This expression is minimal

Practice Exercise # 2

Find the minimal logic expression for:

$$f_4 = \overline{x_1}.\overline{x_2}.\overline{x_3} + \overline{x_1}.\overline{x_2}.x_3 + \overline{x_1}.x_2.\overline{x_3} + x_1.\overline{x_2}.\overline{x_3} + x_1.\overline{x_2}.x_3$$

Also, quantify the benefits of minimization for this example in terms of reduction in number of logic gates

Practice Exercise # 2

Find the minimal logic expression for:

$$f_4 = \overline{x_1}\overline{x_2}\overline{x_3} + \overline{x_1}\overline{x_2}x_3 + \overline{x_1}x_2\overline{x_3} + x_1\overline{x_2}\overline{x_3} + x_1\overline{x_2}x_3$$

Also, quantify the benefits of minimization for this example in terms of reduction in number of logic gates

Solution: $f_4 = \overline{x_2} + \overline{x_1} \cdot \overline{x_3}$

NAND function

Logic
Symbol



NAND function is logically equivalent
to NOT(AND)

x1	x2	$f(x1, x2) = x1 \uparrow x2$
0	0	1
0	1	1
1	0	1
1	1	0

- NAND function is represented by the “ \uparrow ” symbol:

$$f = x1 \uparrow x2$$

- Basic properties of NAND operation:

$$x1 \uparrow x2 = \overline{x1.x2} = \overline{x1} + \overline{x2}$$

$$1 \uparrow x = \overline{x}$$

$$0 \uparrow x = 1$$


$$x \uparrow x = \overline{x}$$

De Morgan's
Law

- Extendible to n variables: $x1 \uparrow x2 \uparrow \dots \uparrow xn = \overline{x1.x2\dots xn} = \overline{x1} + \overline{x2} + \dots + \overline{xn}$

NOR function

Logic
Symbol

 

NOR function is logically equivalent to NOT(OR)

x1	x2	$f(x1, x2) = x1 \downarrow x2$
0	0	1
0	1	0
1	0	0
1	1	0

- NOR function is represented by the “ \downarrow ” symbol:

$$f = x1 \downarrow x2$$

- Basic properties of NOR operation:

$$x1 \downarrow x2 = \overline{x1 + x2} = \overline{x1} \cdot \overline{x2}$$

$$1 \downarrow x = 0$$

$$0 \downarrow x = \overline{x}$$

$$x \downarrow x = \overline{x}$$

De Morgan's
Law



- Extendible to n variables: $x1 \downarrow x2 \downarrow \dots \downarrow xn = \overline{x1 + x2 + \dots + xn} = \overline{x1} \cdot \overline{x2} \cdot \dots \cdot \overline{xn}$

Logic Design with NAND/NOR gates

- Any logic function can be synthesized by using only NAND gates (or NOR gates)
- Procedure
 - Express the logic function in sum-of-products form
 - Apply involution and De Morgan's rules recursively
 - End result is a NAND-NAND network
- Example:

$$\begin{aligned} & x_1x_2 + x_3x_4 \\ &= \overline{\overline{x_1x_2}} + \overline{\overline{x_3x_4}} \\ &= \overline{(\overline{x_1x_2})(\overline{x_3x_4})} \\ &= (x_1 \uparrow x_2) \uparrow (x_3 \uparrow x_4) \end{aligned}$$

  Equivalence of NAND-NAND and AND-OR Networks



These three networks are equivalent

