

# **ECE 341**

## **Lecture # 4**

**Instructor: Zeshan Chishti**  
**zeshan@ece.pdx.edu**

**October 8, 2014**


**Portland State University**

# Lecture Topics


- Decoders
- Multiplexers
- Programmable Logic Devices (PLDs)
  - General Structure of PLDs
  - PLA
  - PAL
  - CPLD
- Reference:
  - Appendix A: Sections A.9 to A.12
 
# Decoder


- Decoder is used to decode encoded information
- A decoder has  $n$  data inputs and  $2^n$  outputs
- For any input data combination, a unique output line has logic value 1 and all the other outputs have the value 0 (one-hot encoding)
- Example: Consider an instruction which performs 8 different functions. A 3-bit field may be used to denote 1 out of the 8 possible functions. A 3-to-8 decoder would decode any instance of the instruction to determine the desired function



# 2-to-4 Decoder Circuit

 


$x_0$	$x_1$	Active Output
0	0	$y_0$
0	1	$y_1$
1	0	$y_2$
1	1	$y_3$

 
 
# BCD to Seven-Segment Display Decoder


- In typical decoders, only one output line asserted for an input combination
- There are other special decoders, where multiple lines may be asserted
- Example: BCD (binary-coded decimal) to seven-segment display decoder
  - Input: a 4-bit BCD digit
  - Output: 7 bits (*a* through *g*) corresponding to 7 display segments
  - Any number from 0 to 9 can be displayed by turning some lights on and others off
  - Multiple outputs may be asserted at once
    - E.g., if input is 0100 (digit 4): *b*, *c*, *f* and *g* are on
  - See Figure A.36 in book for truth table and circuit




# Multiplexer

- A multiplexer (MUX) circuit has:
  - $2^k$  data inputs
  - $k$  select inputs
  - One output
- A MUX passes the signal value on one of its data inputs to the output based on the value of the *select* signals
  - Can be used for gating of data that may come from many different sources

**Multiplexer  
Symbol**

 

# A 4-Input Multiplexer

 

$w_0$	$w_1$	$z$
0	0	$x_0$
0	1	$x_1$
1	0	$x_2$
1	1	$x_3$


$$z = x_0 \overline{w_0} \overline{w_1} + x_1 \overline{w_0} w_1 + x_2 w_0 \overline{w_1} + x_3 w_0 w_1$$

- Logic circuit implementation shown in Figure A.37
- Example usage: A register can be loaded from one of four distinct sources by using a 4-input MUX

# Logic Functions using MUXes

- MUXes can be used to synthesize logic functions
- Example: Consider a function  $f$  of 3 input variables  $x_0$ ,  $x_1$  and  $x_2$  defined by following truth table. This function can be synthesized with a 4-input mux

$x_0$	$x_1$	$x_2$	$f$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

 


$x_0$	$x_1$	$f$
0	0	0
0	1	$x_2$
1	0	1
1	1	$\text{NOT}(x_2)$



# Logic Functions using MUXes

- MUXes can be used to synthesize logic functions
- Example: Consider a function  $f$  of 3 input variables  $x_0$ ,  $x_1$  and  $x_2$  defined by following truth table. This function can be synthesized with a 4-input mux

$x_0$	$x_1$	$x_2$	$f$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

 

# Practice Problem


- Synthesize the function  $f_1$  in the following truth table by using a 4-input mux with  $y_1$  and  $y_2$  as selector inputs.

$y_0$	$y_1$	$y_2$	$f_1$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

# Solution

- Transform the truth table to use  $y_1$  and  $y_2$  as inputs

$y_0$	$y_1$	$y_2$	$f_1$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


$y_1$	$y_2$	$f_1$
0	0	0
0	1	1
1	0	NOT( $y_0$ )
1	1	1


# Solution

- 4-input MUX with  $y_1$  and  $y_2$  as selector inputs

$y_0$	$y_1$	$y_2$	$f_1$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


# Programmable Logic Devices (PLDs)

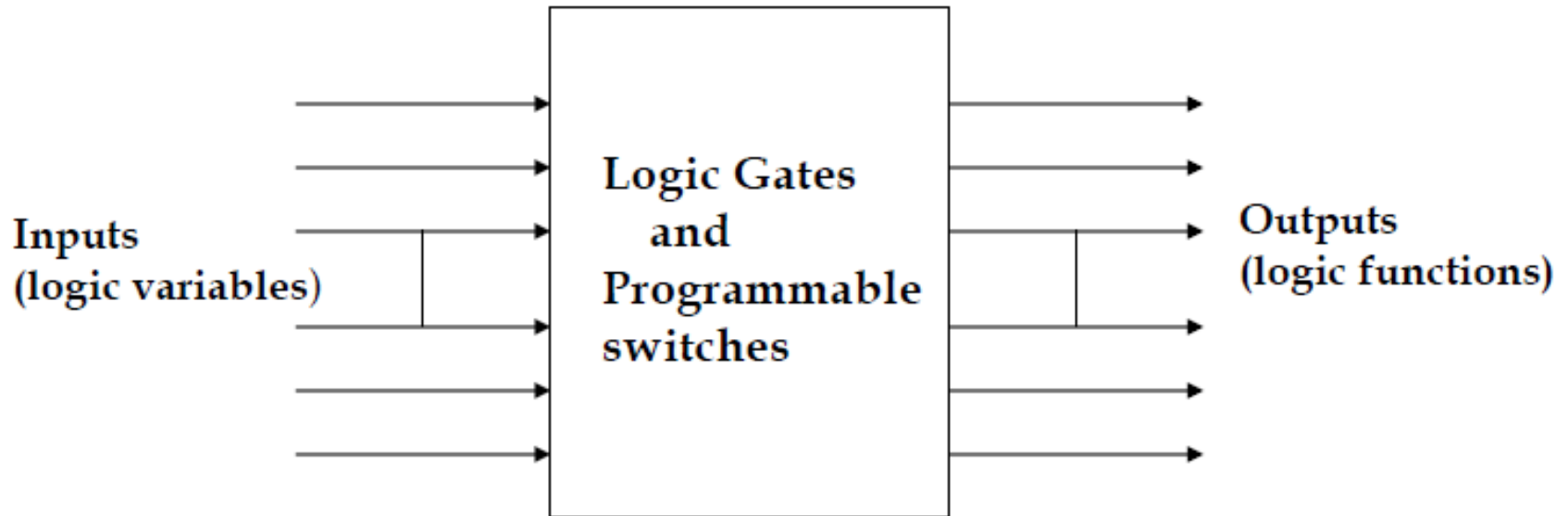

A PLD is a customizable device that can be programmed with switches to implement a variety of combinational functions

# General Structure of PLD

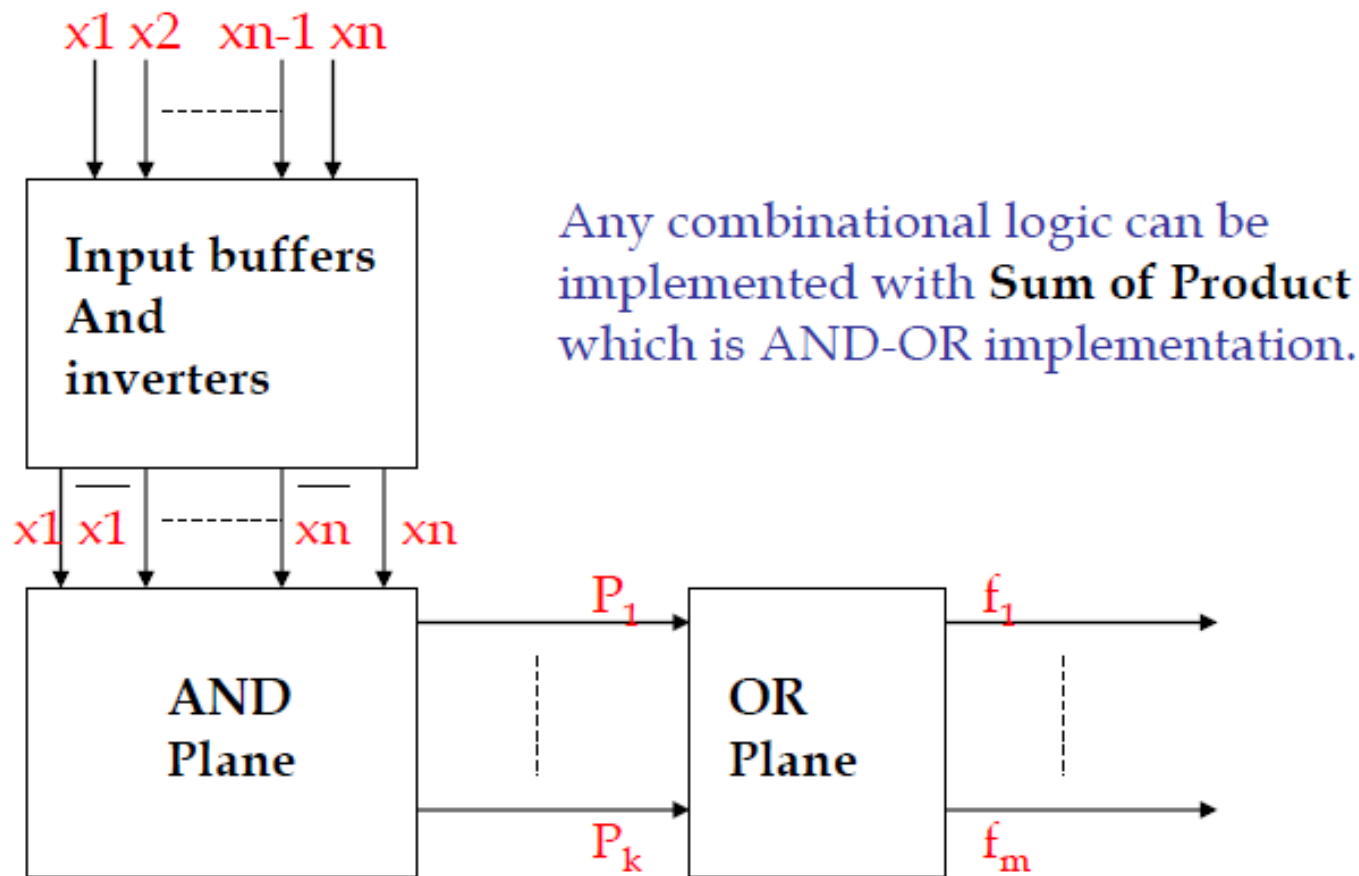


To make a PLD customizable, AND/OR arrays may use programmable switches

# PLD Functionality Table

AND	OR	Device
Fixed	Fixed	Not Programmable
Fixed	Programmable	PROM
Programmable	Fixed	PAL
Programmable	Programmable	PLA

We will focus only on PLA and PAL

# Programmable Logic Array (PLA)

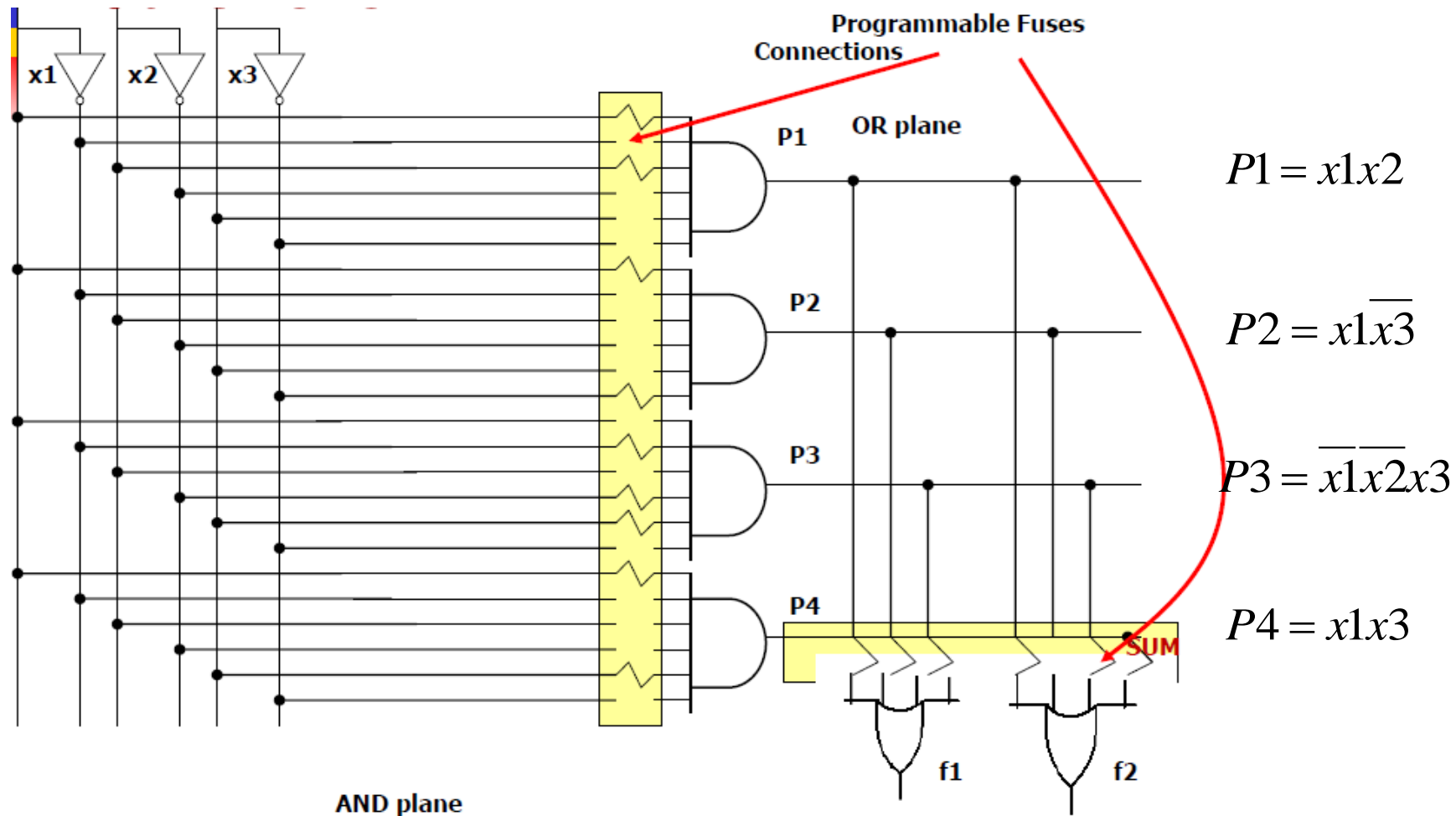


$$f_1 = x_1.x_2 + x_1.\bar{x}_3 + \bar{x}_1.\bar{x}_2.x_3$$

$$f_2 = x_1.x_2 + \bar{x}_1.\bar{x}_2.x_3 + x_1.x_3$$



# PLA in Simplified Form

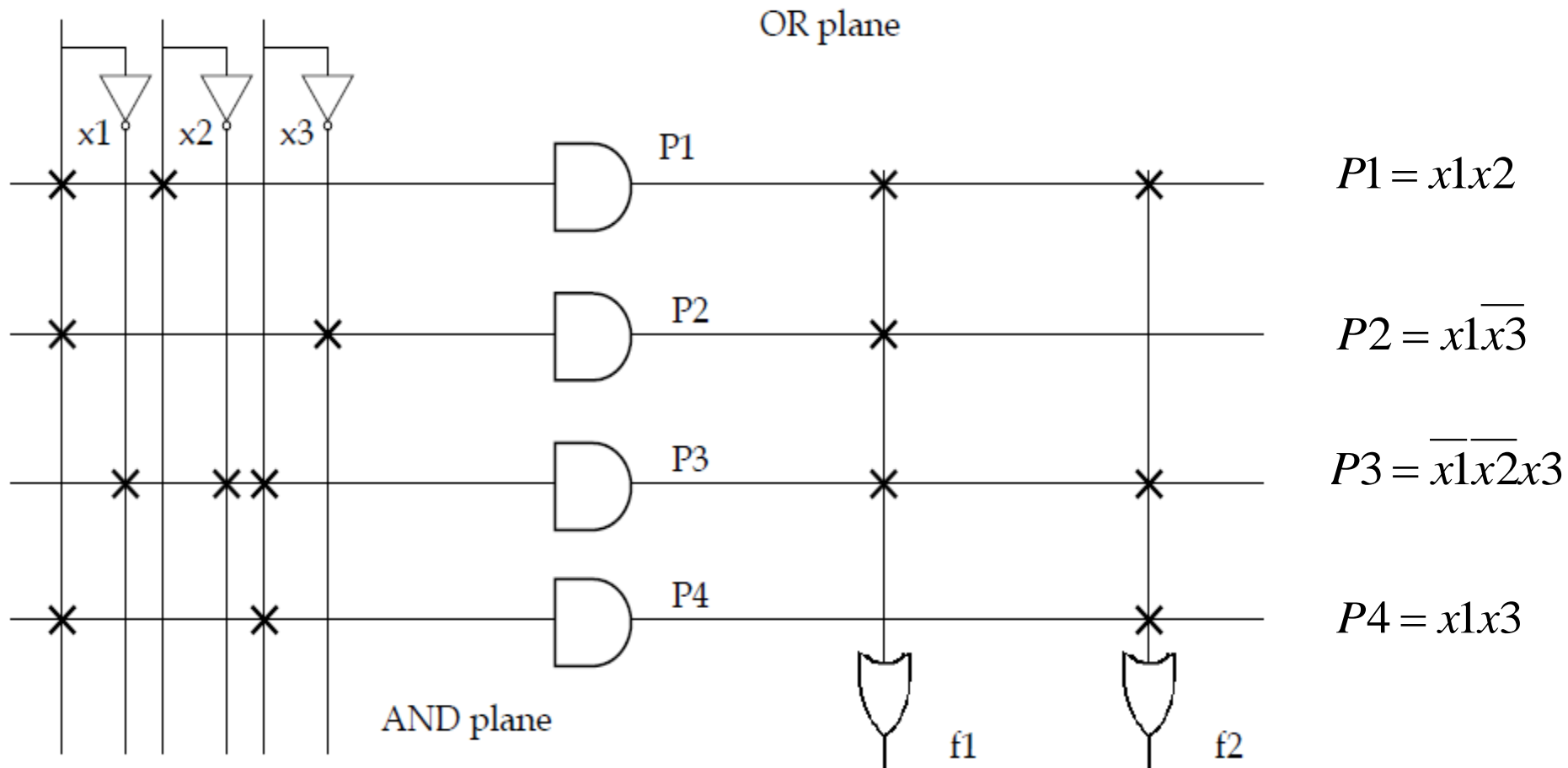


$$f1 = x1.x2 + x1.\bar{x3} + \bar{x1}.\bar{x2}.x3$$

$$f2 = x1.x2 + \bar{x1}.\bar{x2}.x3 + x1.x3$$

# Programmable Array Logic (PAL)

- PLA: *Both* the AND and OR arrays are *programmable*
- PAL: *Programmable* AND array, *Fixed* OR array
  - AND gates permanently connected to specific OR gates
    - # of product terms in a function limited by # of AND gates connected to a OR gate
    - Product terms cannot be shared amongst multiple output functions
  - See example of PAL in Figure A.42
- PLA vs. PAL
  - PLA has more programming flexibility
  - PAL is cheaper to implement (less switches)
  - PAL has higher speed (more fixed connections)
- PAL circuits often include flip-flops and MUXes after OR gate outputs to provide additional flexibility (Figure A.43)
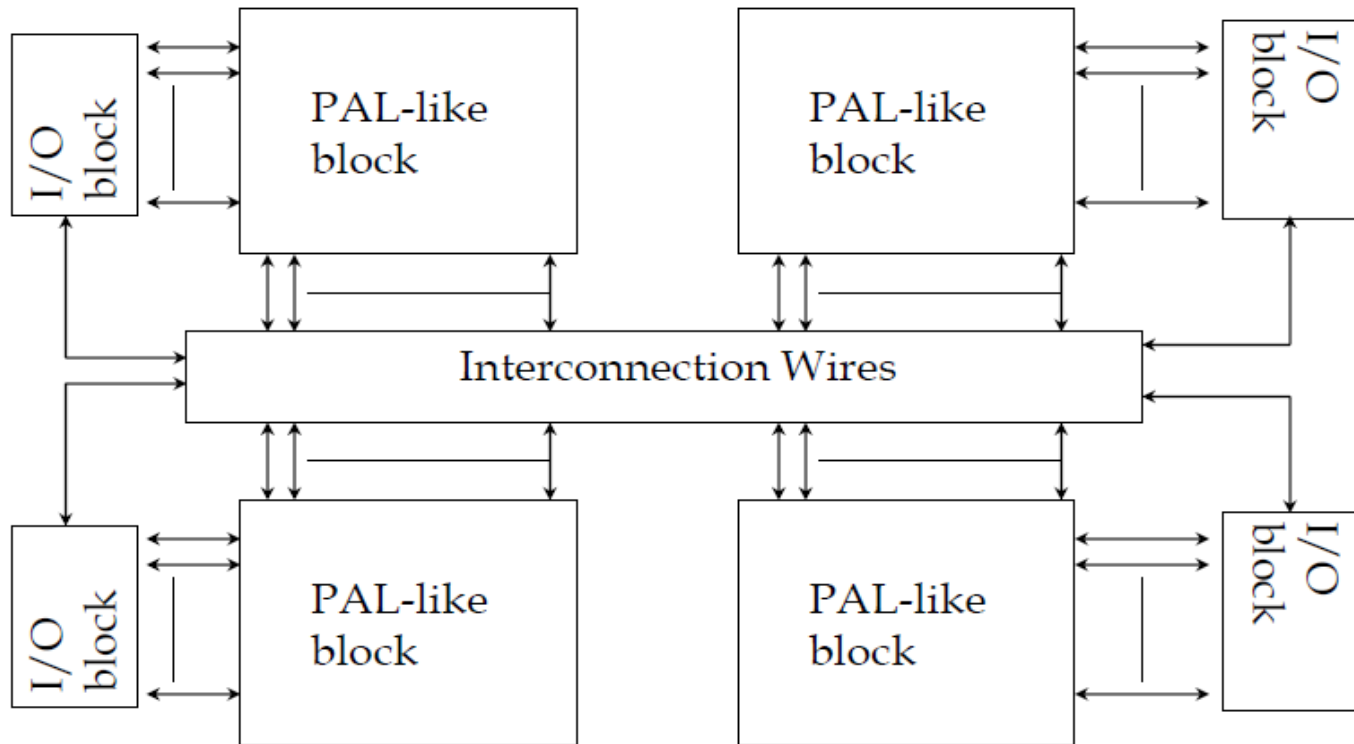
# Complex Programmable Logic Devices (CPLDs)



- Connections between PAL blocks established by programming interconnect switches
- Programming information loaded via JTAG port
- CAD tools often used to program large CPLDs

# Programmable vs. Custom Devices

- Programmable devices, such as CPLDs and field-programmable gate arrays (FPGAs) can be configured to implement a *variety* of complex logic circuits
- Specialized devices, such as Application-Specific Integrated Circuits (ASICs) are designed *specifically* for a particular operation, e.g., MPEG decode
- There is a tradeoff between programmability and cost/performance/energy efficiency
- CPLDs/FPGAs are more programmable
  - Faster design times
  - Less development cost
- ASICs are tuned for a specific task
  - Higher performance
  - Better energy efficiency