

ECE 341

Lecture # 10

Instructor: Zeshan Chishti
zeshan@ece.pdx.edu


October 29, 2014

Portland State University

Lecture Topics


- Basic Processing Unit
 - Hardware Components
 - Register File
 - ALU
 - Datapath
 - Instruction Fetch Section
 - Instruction Fetch and Execution Steps
 - Instruction Encoding
 - Examples
- Reference:
 - Chapter 5: Sections 5.3 and 5.4 (Pages 161-168 of textbook)

Hardware Components of a Processor

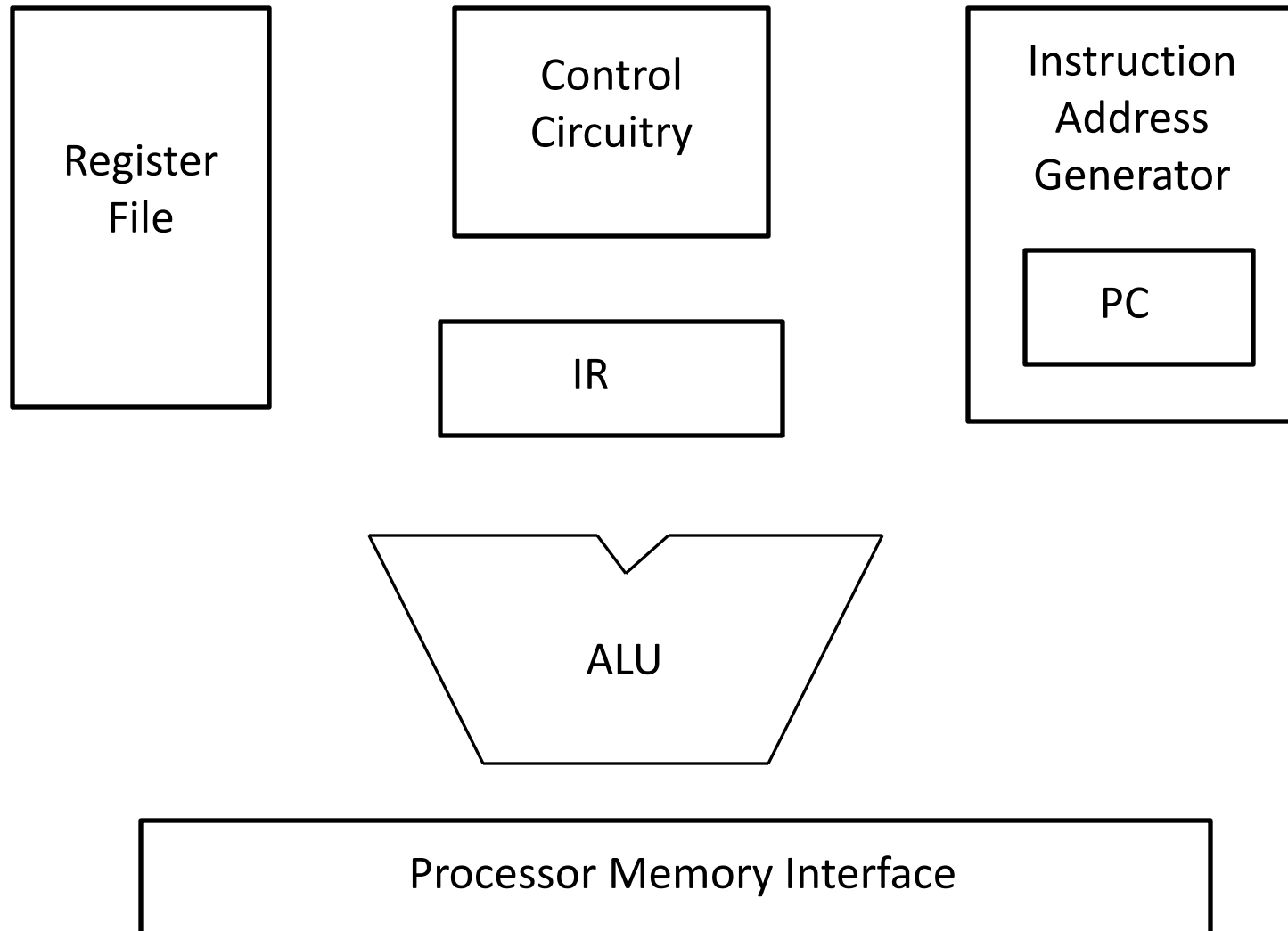


Register File

- General purpose registers are usually implemented as a *register file*
- Register file contains
 - Array of storage elements to hold register contents
 - Access circuitry to read/write data from/into any register
- To support two source operands per instruction
 - Access circuitry able to read 2 registers at same time
 - Address inputs *A* & *B* select the registers to be read
 - Address inputs connected to *IR's source register fields*
 - Register contents available at separate outputs
- To support a destination operand
 - Address input *C* selects the register to be written
 - *C* is connected to *IR's destination register field*
 - Data input used to specify the data to be written
- For example, for instruction add R3, R4, R5
 - *A* = 4, *B* = 5 and *C* = 3

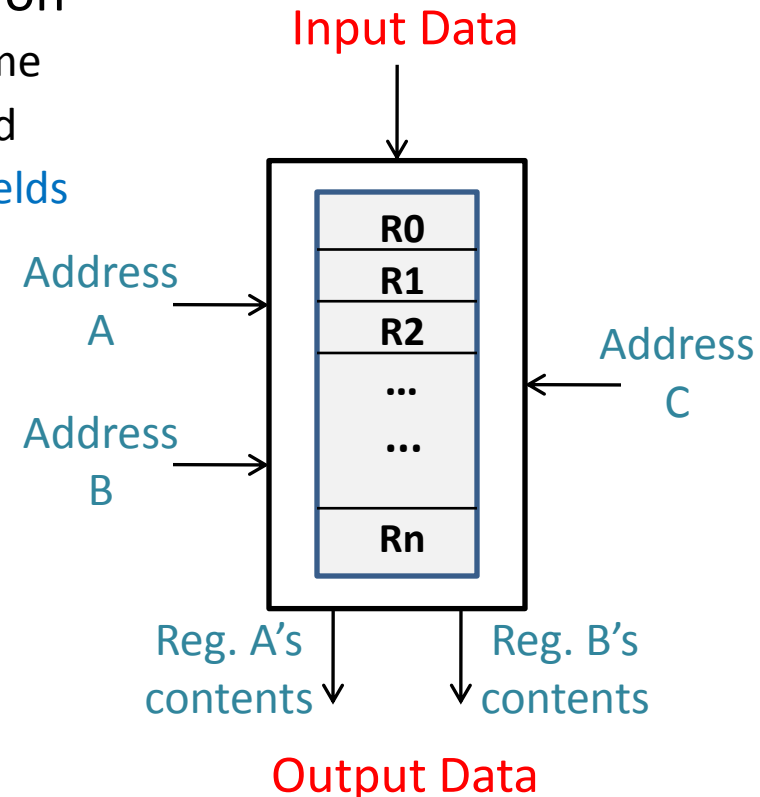

Register File (cont.)

- A memory unit with two output ports is said to be *dual ported*
- Two ways to implement a **dual-ported register file**
- **True ports:** Single set of registers with duplicate data paths and access circuitry that enables two registers to be read at a time
- **Two copies:** Use 2 memory blocks each containing one copy of the register file
 - To read two registers, one register can be accessed from each file
 - To write a register, data needs to be written to both the copies of that register

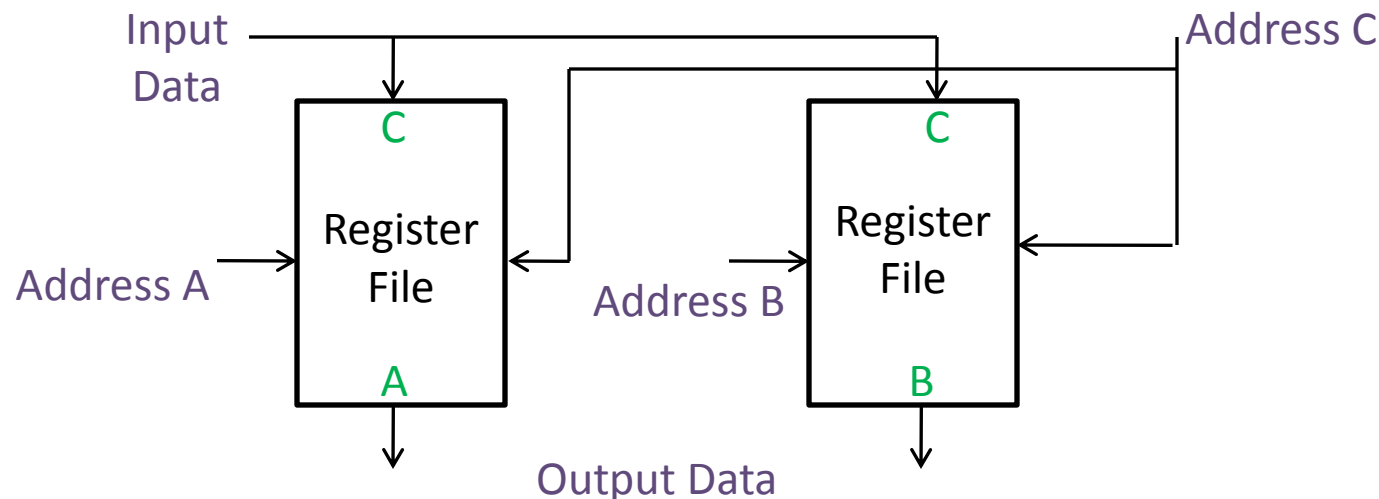


ALU


- Arithmetic and Logic Unit (ALU) performs:
 - Arithmetic operations (addition, subtraction, multiplication etc.)
 - Logic operations (bitwise AND, OR, XOR etc.)
- Register file and ALU are connected with each other so that
 - Source operands of an instruction, after being read from the register file are directly fed into the ALU
 - Result computed by the ALU can be loaded into the destination register specified by the instruction

ALU + Register File Connection

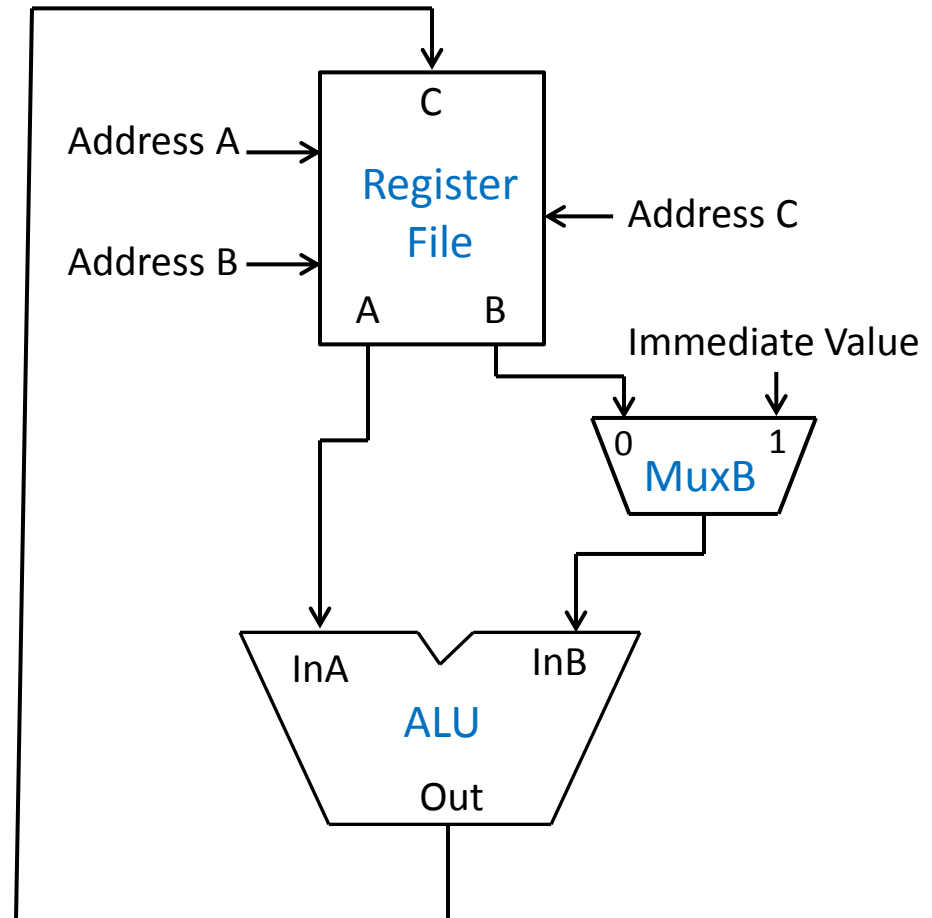- Source register *A* connected to *InA* input of ALU
- Multiplexer MuxB connected to *InB* input of ALU and the *immediate value* field in IR
 - MuxB selects *InB*, for operations that require only register operands
 - MuxB selects *immediate value* for operations that require an immediate operand




Hardware Components of a Processor

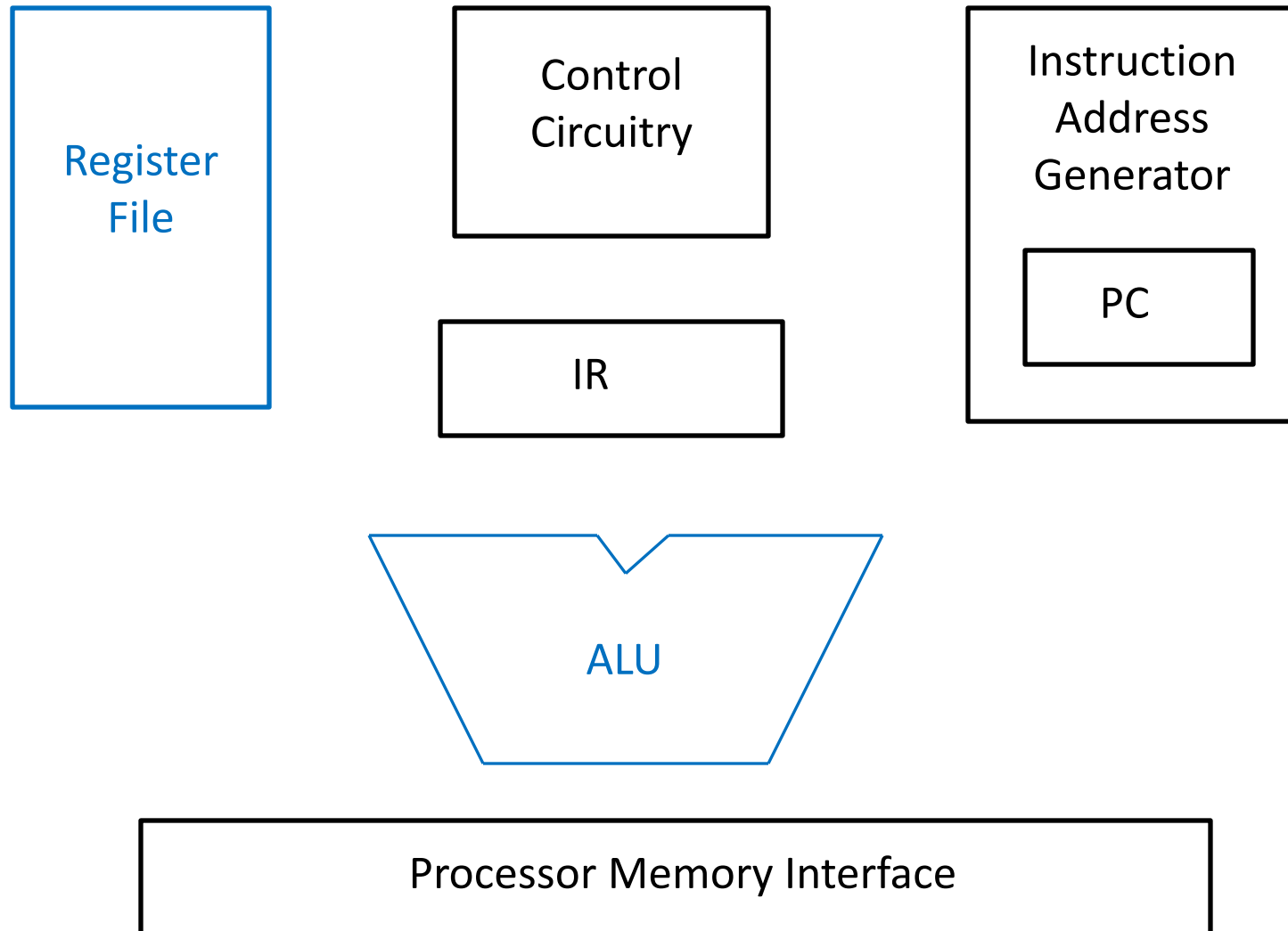


Datapath

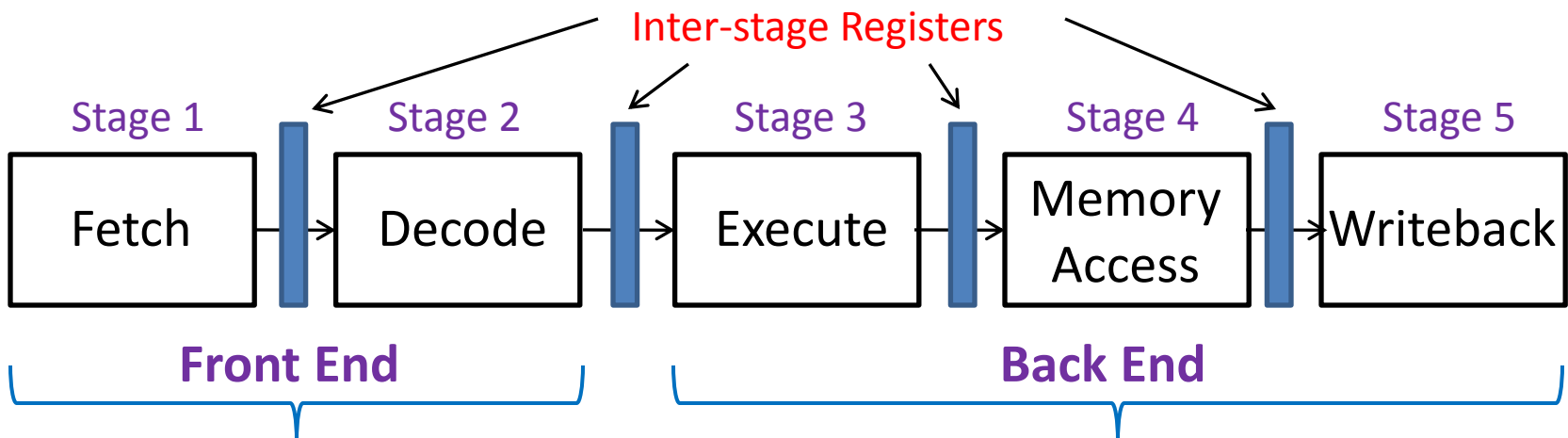- Recall that instruction processing consists of *fetch phase* & *execution phase*
- Processor hardware divided into two corresponding sections:
 - Front end (fetch section):**
 - Includes the fetch and decode stages
 - Back end (execute section):**
 - Includes the ALU, Memory Access and Writeback stages
- Datapath** is a combination of register read, back-end stages and inter-stage registers



RA, RB, RZ, RM and RY
are **inter-stage**
registers

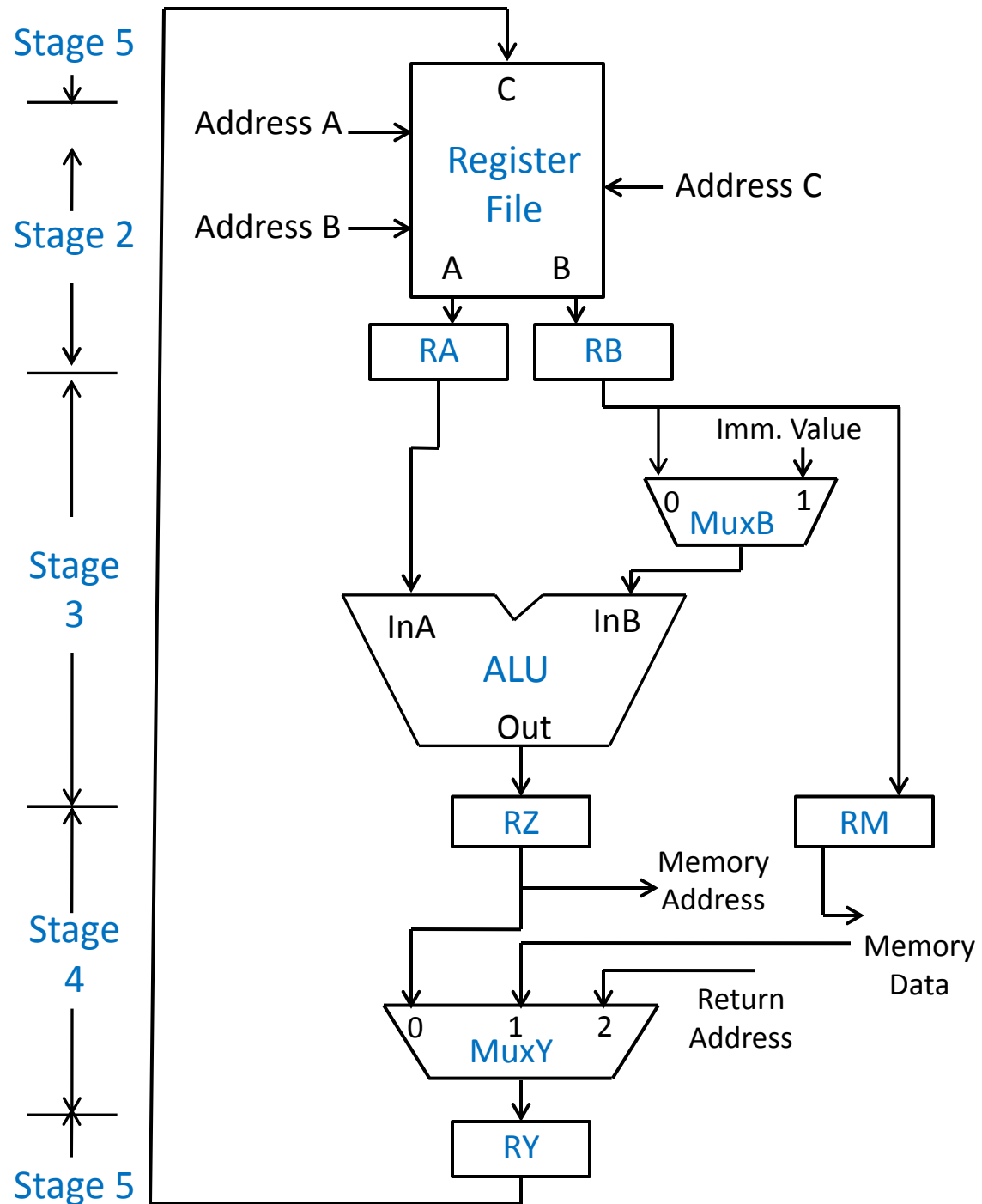Register file is in both
stage 2 and stage 5,
because stage 2 (Decode)
reads source registers and
stage 5 (Writeback) writes
into destination registers



Arithmetic/Logic Instructions:

Instruction Type	MuxB selection	MuxY selection
1 source register, 1 immediate operand	1	0
2 source registers	0	0

- **Stage 3:** ALU carries out the desired arithmetic/logic operation on the source operands, result is loaded into RZ
- **Stage 4:** Result computed in stage-3 moves from RZ to RY
- **Stage 5:** Data transferred from RY into destination


Stage 5

Stage 2

Stage 3

Stage 4

Stage 5

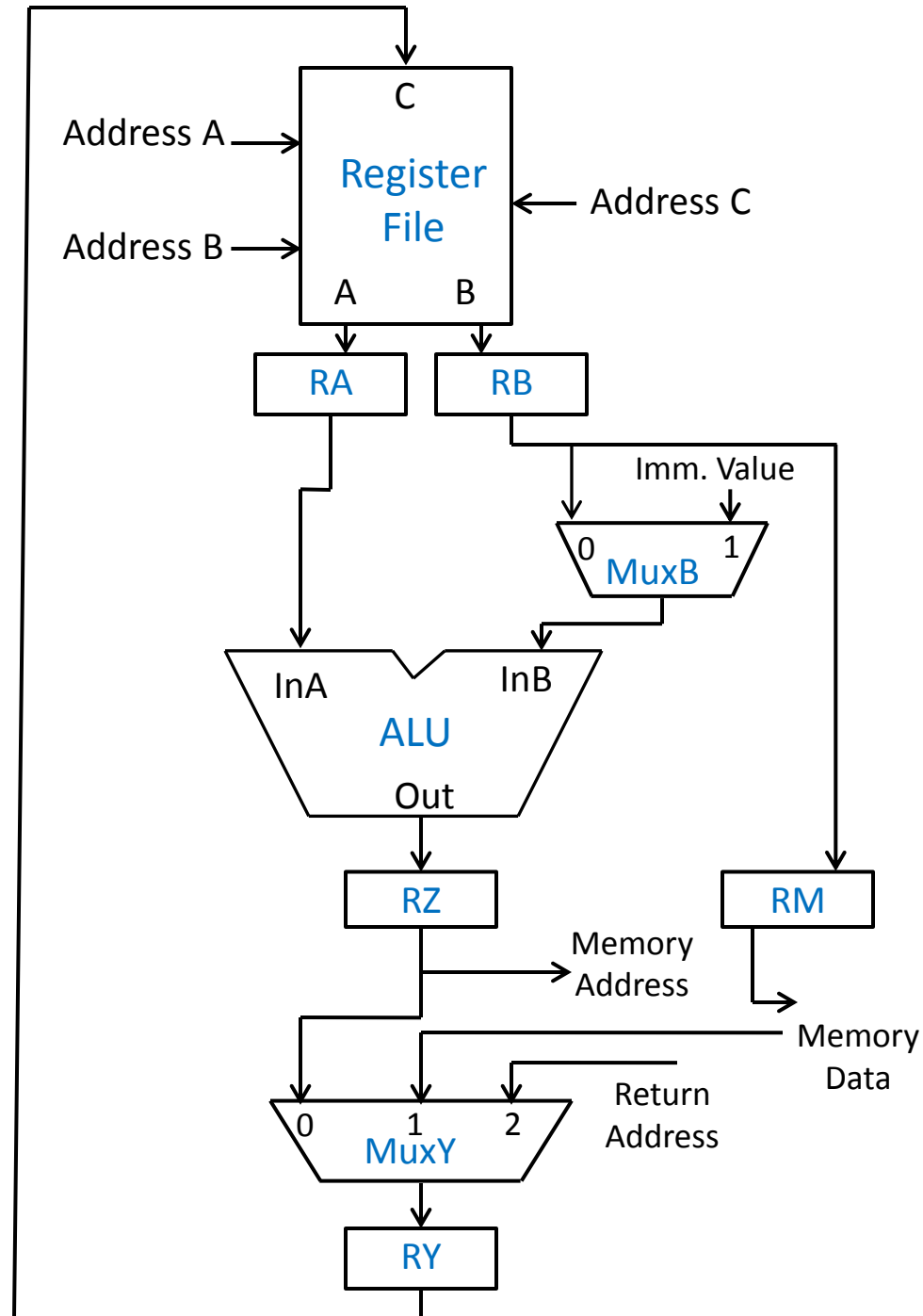


Load Instructions:


Instruction Type	MuxB selection	MuxY selection
Load	1	1

- **Stage 3:** Effective address computed and loaded into RZ
- **Stage 4:** Address sent from RZ to memory, data returned by memory loaded into RY
- **Stage 5:** Data transferred from RY into destination

Stage 5

 

Stage 2

 


Stage 3



Stage 4




Stage 5

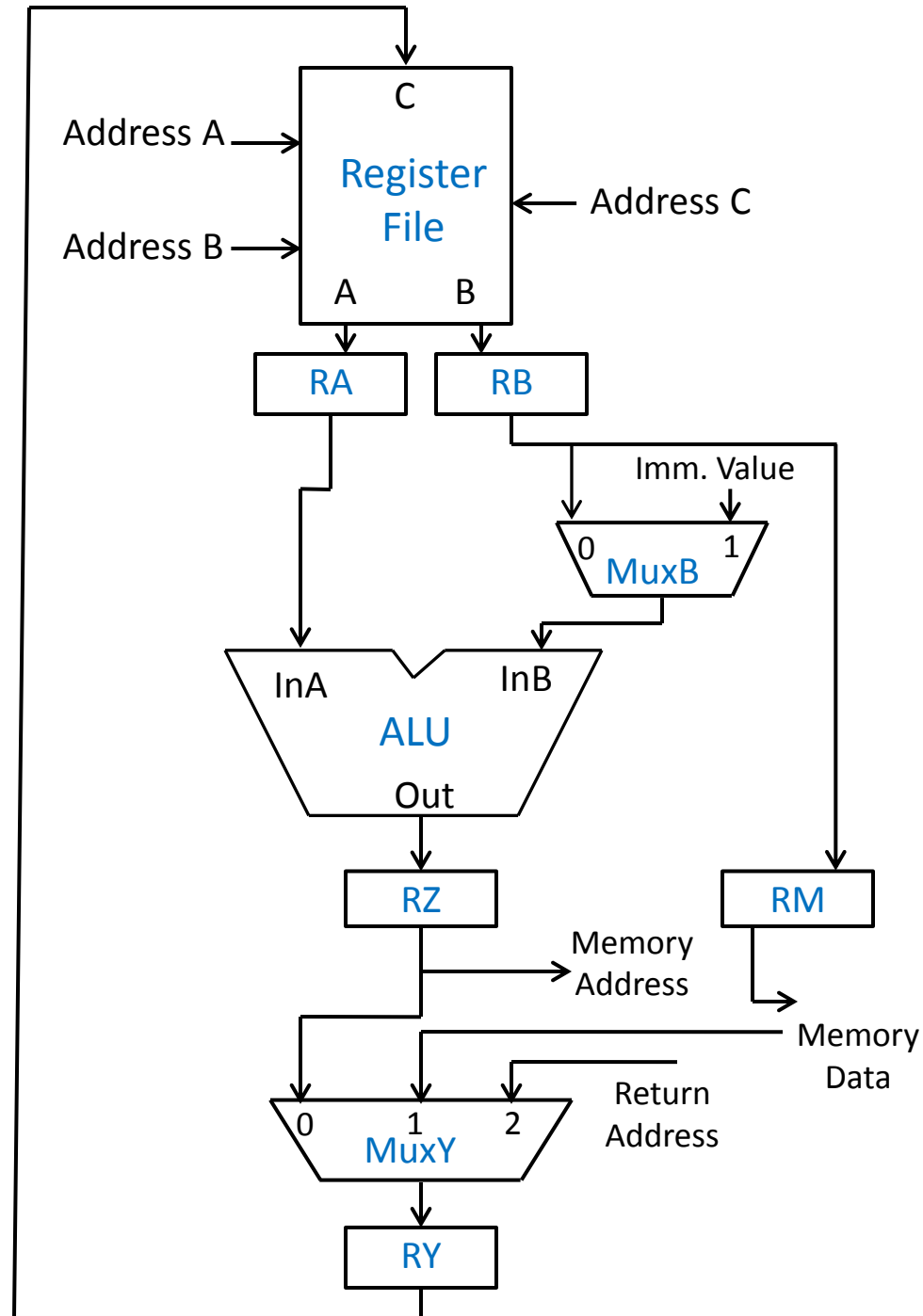

Store Instruction:

Instruction Type	MuxB selection	MuxY selection
Store	1	x

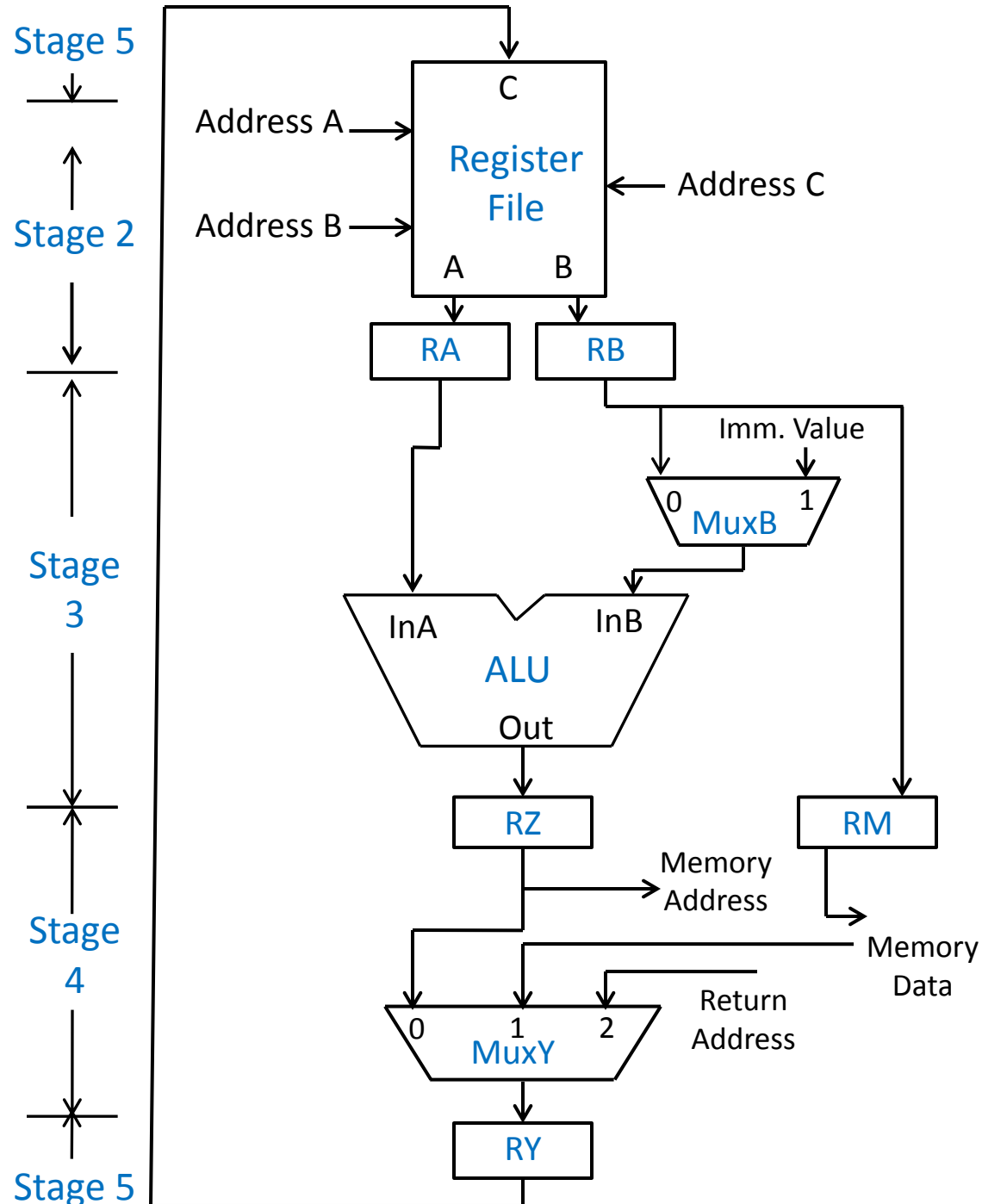- **Stage 3:** Effective address computed and loaded into RZ, data to be stored is moved from RB to RM
- **Stage 4:** Address sent from RZ to memory, data sent from RM to memory, write signal asserted
- **Stage 5:** No action




Subroutine Call Instruction:

saves the subroutine return address (current contents of PC) in a destination register

Instruction Type	MuxB selection	MuxY selection
Subroutine Call	x	2

- **Stage 3:** No action
- **Stage 4:** Return address sent from PC to RY
- **Stage 5:** Contents of RY sent to the destination register


Stage 5

 

Stage 2




Stage 3

 


Stage 4



Stage 5

 


Stage 4

 

Stage 5




Stage 5

 


Stage 5




Stage 5

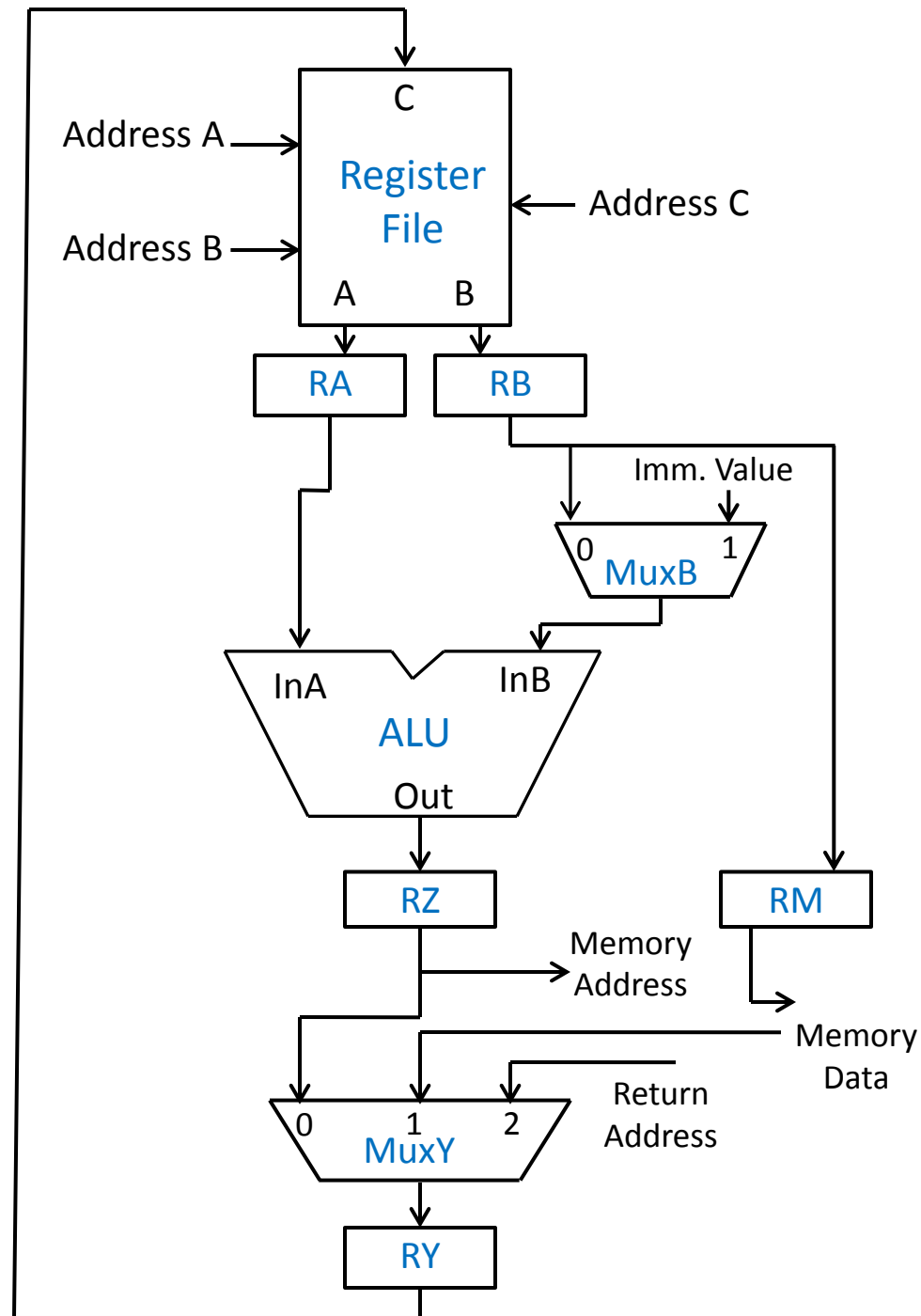


Hardware Components of a Processor

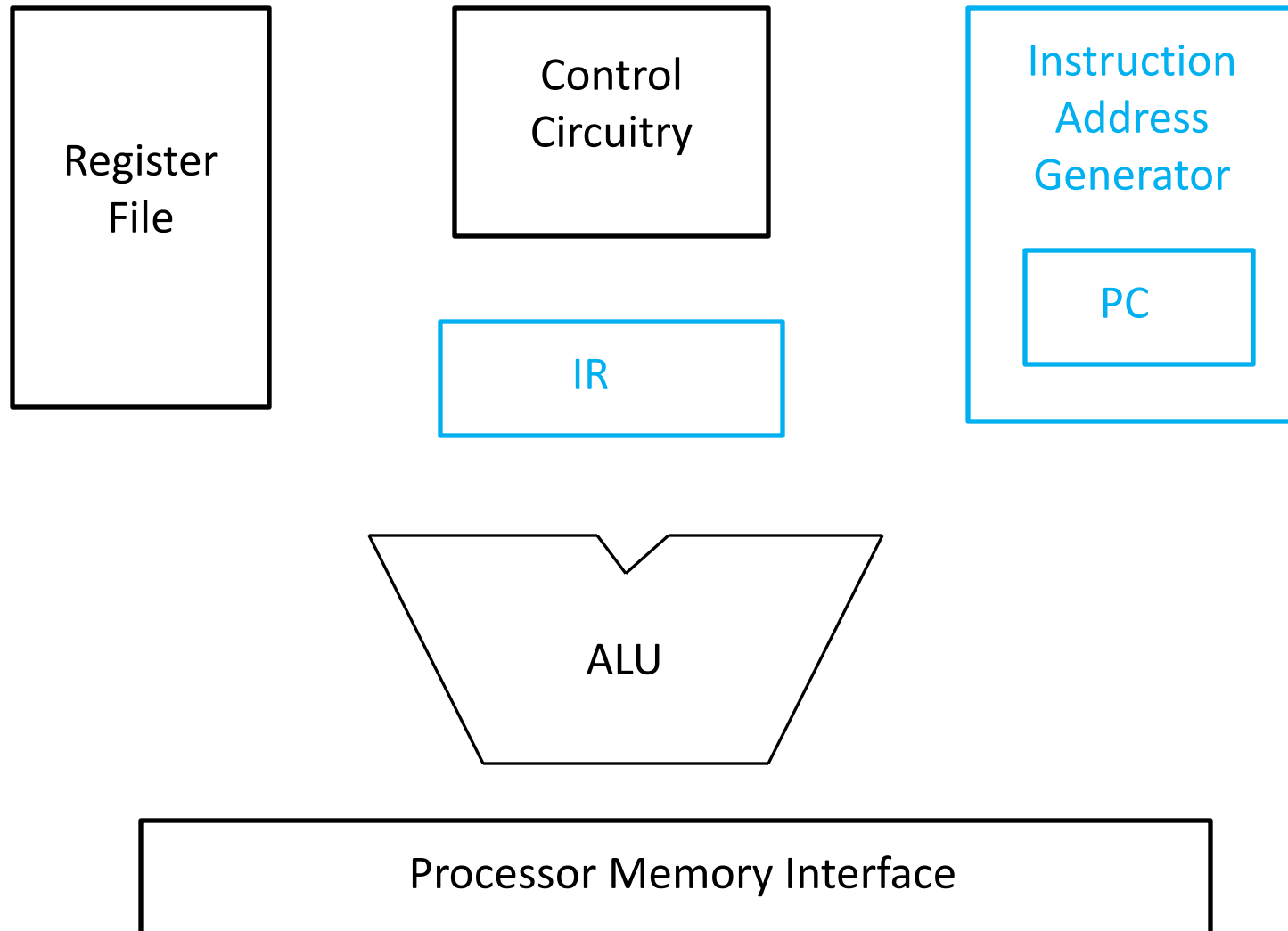

Instruction Fetch Step

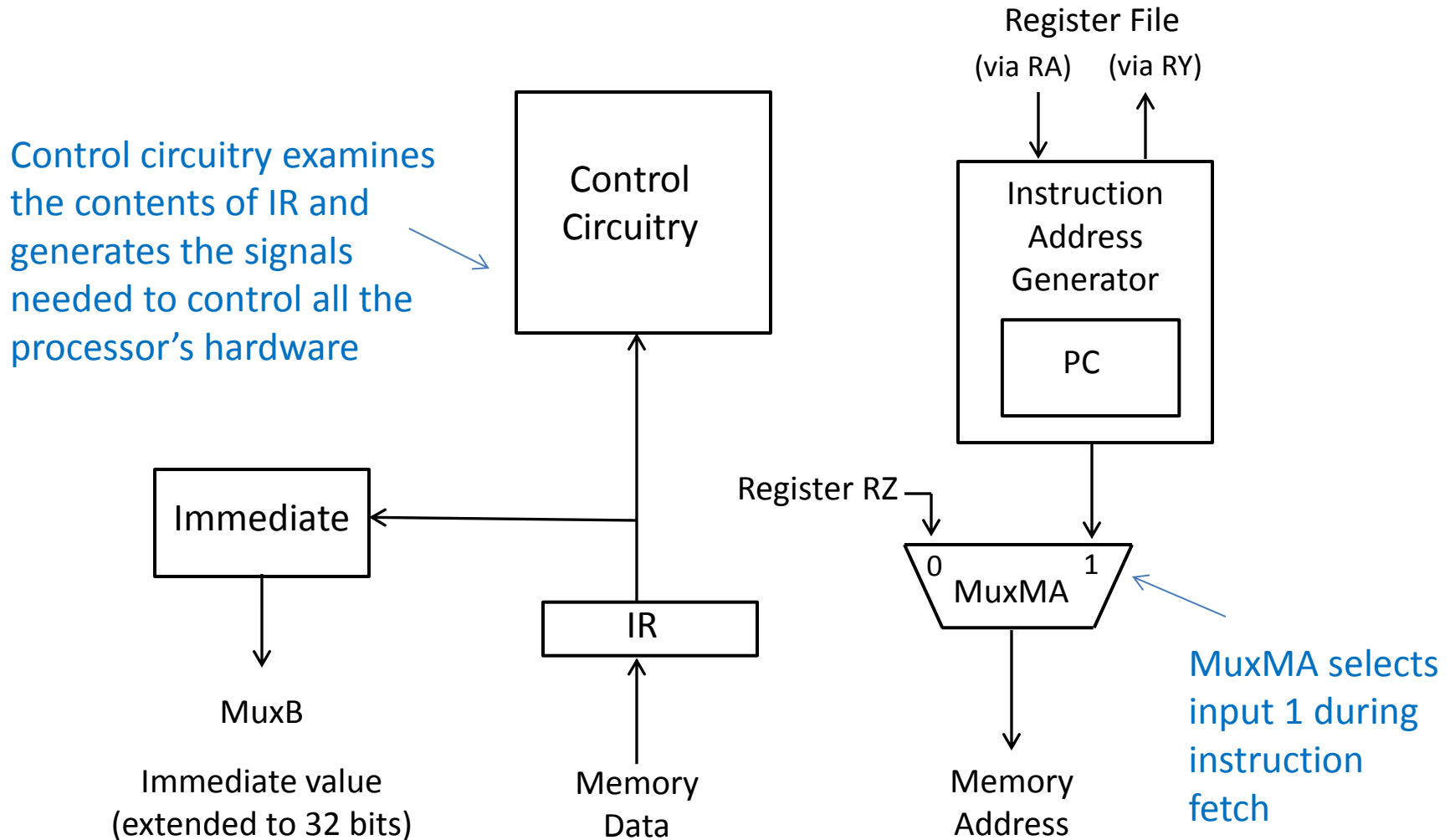


Instruction Address Generator

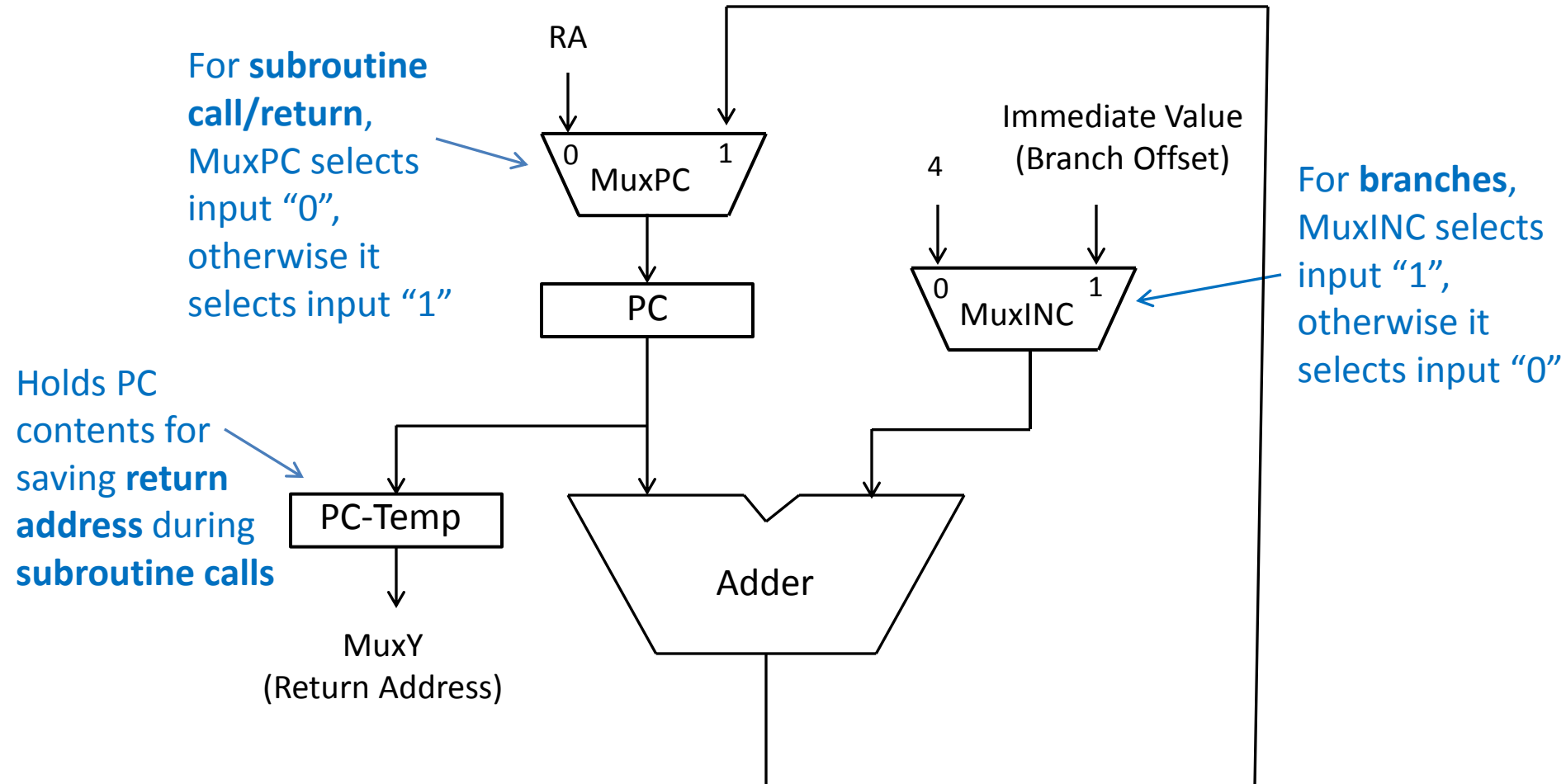


Immediate Field Extension

- Immediate operand needs to be represented as a 32-bit number before being used as ALU's input
- “Immediate” block extends the *immediate* field in IR and sends the extended value to MuxB
- For logical instructions (AND, OR etc.)
 - Immediate value is padded with zeroes to extend from 16 to 32 bits
- For arithmetic instructions (add, mult etc.) and branches
 - Immediate value is sign-extended from 16 to 32 bits


Instruction Encoding

 

(a) Register-operand format

 

(b) Immediate-operand format

 

(c) Call format

Using a few standard instruction formats simplifies the instruction decoding process

Instruction Encoding (cont.)

- The **OP code** field specifies the type of instruction
 - Control circuitry examines the op code to decide which control signals to assert in subsequent stages
- Can the reading of source registers proceed, while the control circuitry is yet to decode the instruction op code?
- **YES**, because source register addresses are specified using the same bit positions in all instructions (bits 31-27 and bits 26-22)
 - These two fields in IR (IR[31-27] and IR[26-22]) are connected to address inputs A and B of register file
 - **Contents of these two registers are loaded into RA and RB at the end of stage 2, irrespective of the type of instruction**
 - If these contents are not needed, subsequent stages can ignore them
 - If needed, these contents will be available as operands in stage 3

Example 1: Add R3, R4, R5

Stage 1:

Memory address \leftarrow [PC],
Read memory,
IR \leftarrow Memory data,
PC \leftarrow [PC] + 4

Stage 2:

Decode instruction,
RA \leftarrow [R4], RB \leftarrow [R5]

Stage 3:


RZ \leftarrow [RA] + [RB]

Stage 4:

RY \leftarrow [RZ]

Stage 5:

R3 \leftarrow [RY]

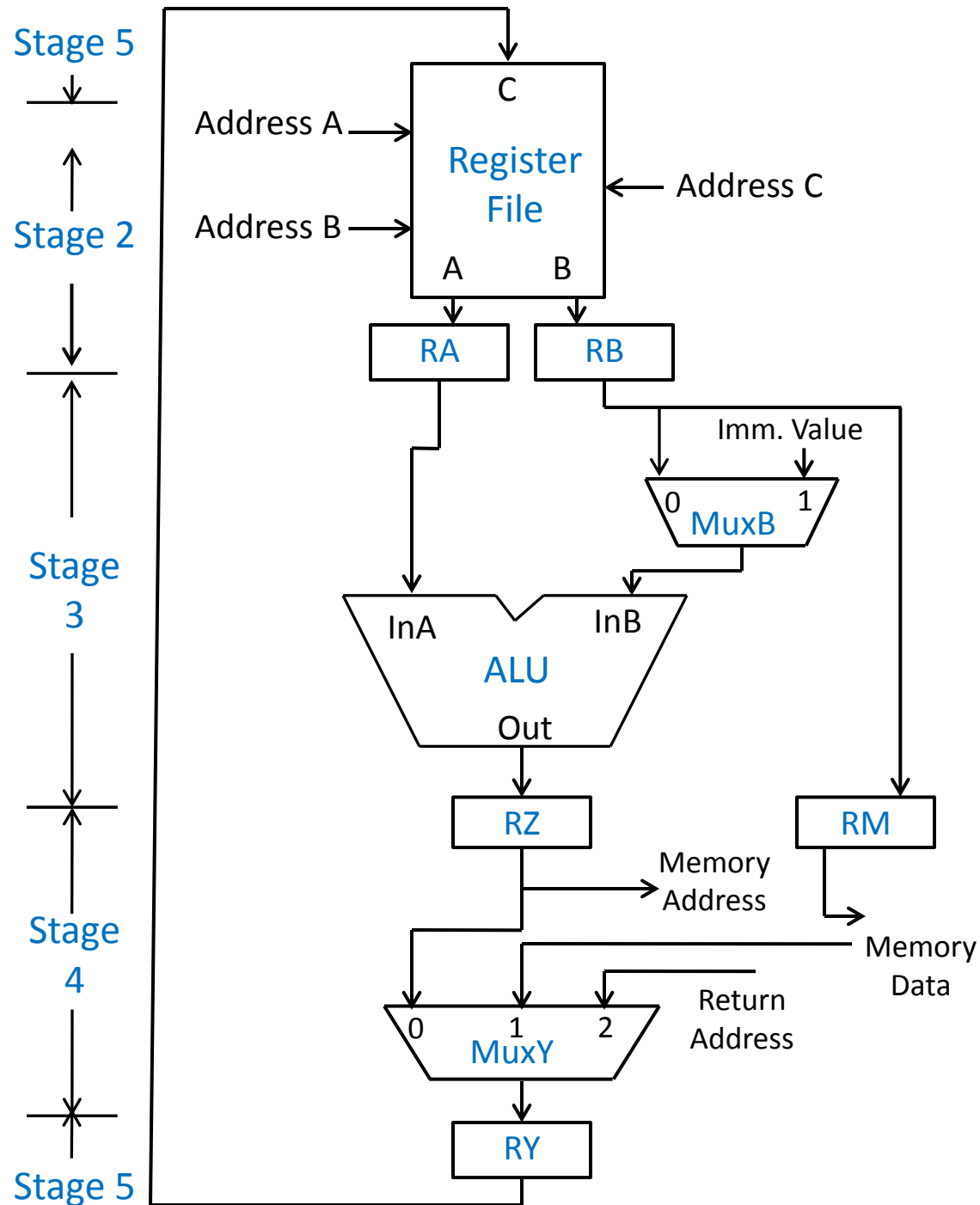

Example 2: Load R5, X(R7)

Stage 1:

Memory address \leftarrow [PC],
Read memory,
IR \leftarrow Memory data,
PC \leftarrow [PC] + 4

Stage 2:

Decode instruction,
RA \leftarrow [R7]

Stage 3:


RZ \leftarrow [RA] + Immediate value X

Stage 4:

Memory address \leftarrow [RZ],
Read memory
RY \leftarrow Memory data

Stage 5:

R5 \leftarrow [RY]

 

Example 3: Store R6,X(R8)

Stage 1:

Memory address \leftarrow [PC],
Read memory,
IR \leftarrow Memory data,
PC \leftarrow [PC] + 4

Stage 2:

Decode instruction,
RA \leftarrow [R8], RB \leftarrow [R6]

Stage 3:

RZ \leftarrow [RA] + Immediate value X
RM \leftarrow [RB]

Stage 4:

Memory address \leftarrow RZ,
Memory data \leftarrow [RM],
Write memory

Stage 5:

No action

