

# **ECE 341**

## **Lecture # 2**

**Instructor: Zeshan Chishti**  
**zeshan@pdx.edu**

**October 1, 2014**

**Portland State University**


# Announcements

- Course website reminder:  
<http://www.ece.pdx.edu/~zeshan/ece341.htm>
- Homework 1:
  - Will be posted on course website tonight
  - Due date: Wednesday 10/8 in class

# Lecture Topics


- Sequential Logic
  - Latches
    - SR Latch
    - Gated SR Latch
    - Gated D Latch
  - Flip flops
    - D flip-flop
    - T flip-flop
    - JK flip-flop
- Reference: Appendix A (pages 492-502), including section A.6

# Sequential Logic

 

- Combinational logic:
  - outputs are uniquely defined for each input combination
- Sequential Logic:
  - output depends not only on current inputs but also on previous state

# Clock Signal

 


- Sequential circuits often use a clock signal as a reference for when output state changes take place
- **Level triggering:** State changes can take place at any time as long as clock signal is at a particular level (e.g., during the “1” clock phase)
- **Edge triggering:** State changes take place only on clock transitions
  - 0 => 1 transition (positive edge-triggered)
  - 1 => 0 transition (negative edge-triggered)

# Latches and Flip Flops

- Latches and flip flops are the most basic memory elements used in sequential circuits
- Flip flop
  - Samples its inputs and changes its output only at the *edge* of a controlling clock signal (edge-triggered)
- Latch
  - Watches its inputs continuously and changes its output *at any time* irrespective of clock edge transitions
  - May or may not be level-triggered

# SR Latch

 


(b)

| S | R | Q      | QN      |
|---|---|--------|---------|
| 0 | 0 | last Q | last QN |
| 0 | 1 | 0      | 1       |
| 1 | 0 | 1      | 0       |
| 1 | 1 | 0      | 0       |

An SR latch has a set input (S), a reset input (R) and two outputs (Q and QN) that are normally complements of each other

# SR Latch

 


(b)

| S | R | Q      | QN      |
|---|---|--------|---------|
| 0 | 0 | last Q | last QN |
| 0 | 1 | 0      | 1       |
| 1 | 0 | 1      | 0       |
| 1 | 1 | 0      | 0       |



# SR Latch

 


(b)

| S | R | Q      | QN      |
|---|---|--------|---------|
| 0 | 0 | last Q | last QN |
| 0 | 1 | 0      | 1       |
| 1 | 0 | 1      | 0       |
| 1 | 1 | 0      | 0       |

$x \text{ NOR } 1 = 0$  for  $x = 0, 1$

# SR Latch

 


(b)

| S | R | Q      | QN      |
|---|---|--------|---------|
| 0 | 0 | last Q | last QN |
| 0 | 1 | 0      | 1       |
| 1 | 0 | 1      | 0       |
| 1 | 1 | 0      | 0       |

$$0 \text{ NOR } 0 = 1$$

# SR Latch

 


(b)

| S | R | Q      | QN      |
|---|---|--------|---------|
| 0 | 0 | last Q | last QN |
| 0 | 1 | 0      | 1       |
| 1 | 0 | 1      | 0       |
| 1 | 1 | 0      | 0       |

- Asserting S *sets* the latch ( $Q = 1$ ,  $QN = 0$ )
- Asserting R *resets* the latch ( $Q = 0$ ,  $QN = 1$ )
- If both S and R are 0, the latch acts as a memory element (retains its previous state)
- Input combination  $R = S = 1$  is normally not used
  - QN is often represented as  $\bar{Q}$  (NOT of Q)


# Gated SR Latch

Circuit

 


| Clk | S | R | $Q(t+1)$ |
|-----|---|---|----------|
| 0   | x | x | $Q(t)$   |
| 1   | 0 | 0 | $Q(t)$   |
| 1   | 0 | 1 | 0        |
| 1   | 1 | 0 | 1        |
| 1   | 1 | 1 | x        |

Truth Table

 

Graphical Symbol


# Gated SR Latch

 


Clock input controls the time at which the latch is set or reset

- When  $clk = 1$ 
  - $R' = R$  and  $S' = S$ , behaves like a regular SR latch set/reset by  $S/R$  inputs)
- When  $clk = 0$ 
  - $R' = S' = 0$ , latch cannot be set or reset by  $R$  and  $S$  inputs

# Timing Diagram for Gated SR Latch

 


# Gated D Latch

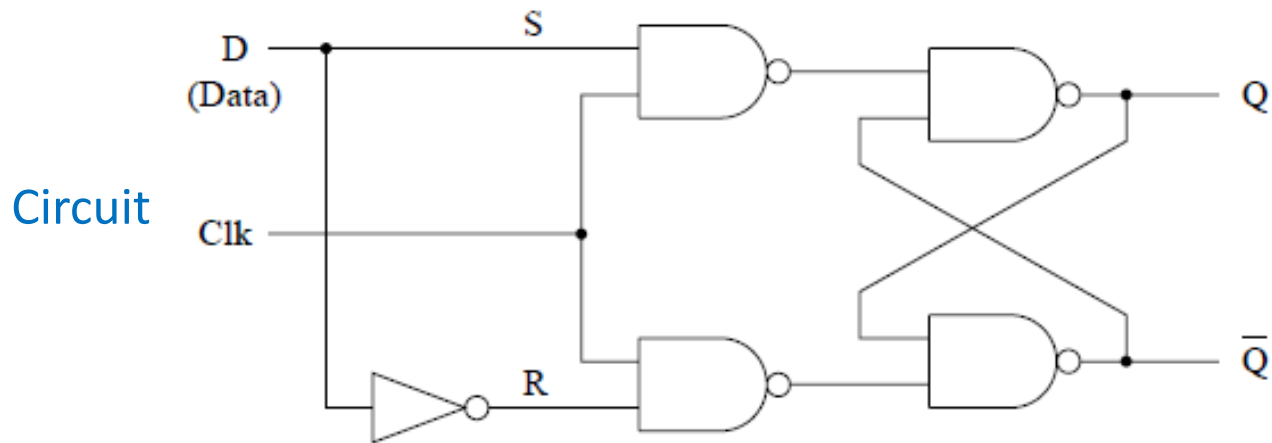


| Clk | D | $Q(t+1)$ |
|-----|---|----------|
| 0   | x | $Q(t)$   |
| 1   | 0 | 0        |
| 1   | 1 | 1        |

Truth Table

 


Graphical Symbol

# Gated D Latch

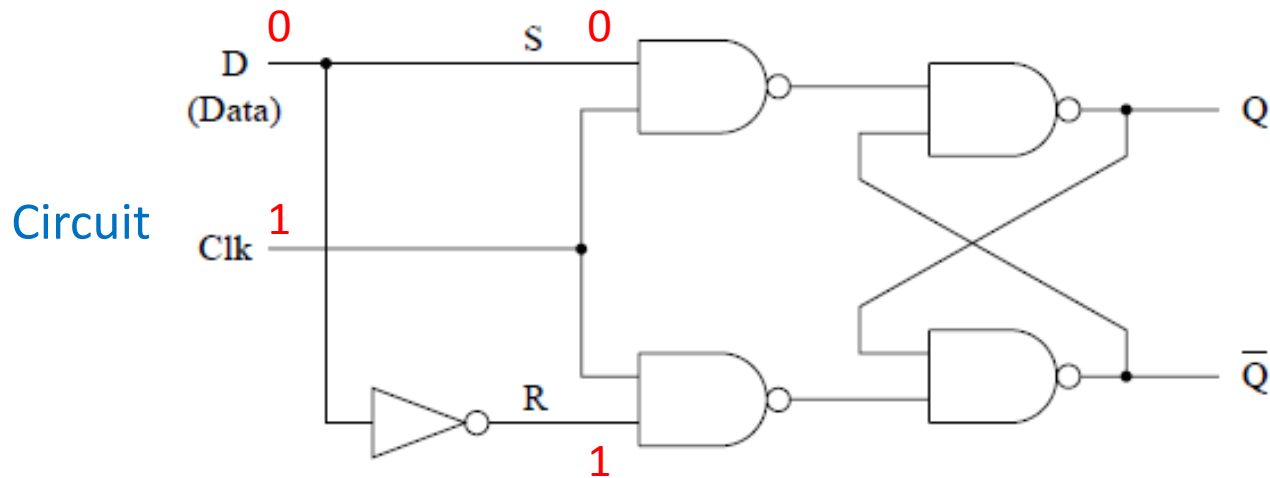

| Clk | D | $Q(t+1)$ |
|-----|---|----------|
| 0   | x | $Q(t)$   |
| 1   | 0 | 0        |
| 1   | 1 | 1        |


Truth Table

 

Graphical Symbol




# Gated D Latch

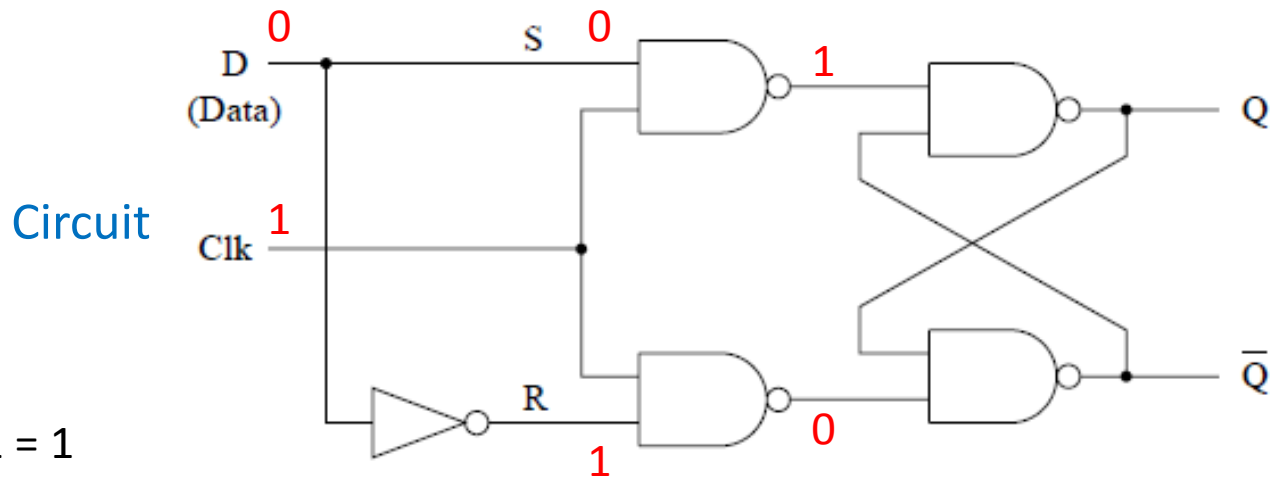

0 NAND 1 = 1  
1 NAND 1 = 0


| Clk | D | $Q(t+1)$ |
|-----|---|----------|
| 0   | x | $Q(t)$   |
| 1   | 0 | 0        |
| 1   | 1 | 1        |

Truth Table

 

Graphical Symbol


# Gated D Latch

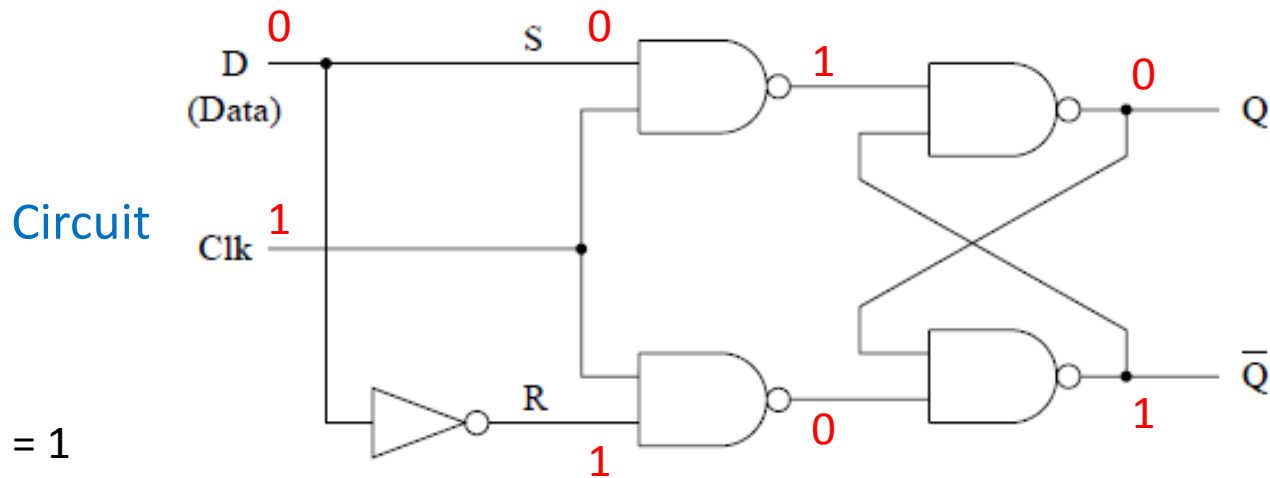

Q NAND 0 = 1  
1 NAND 1 = 0


| Clk | D | Q(t+1) |
|-----|---|--------|
| 0   | x | Q(t)   |
| 1   | 0 | 0      |
| 1   | 1 | 1      |

Truth Table

 

Graphical Symbol

# Gated D Latch

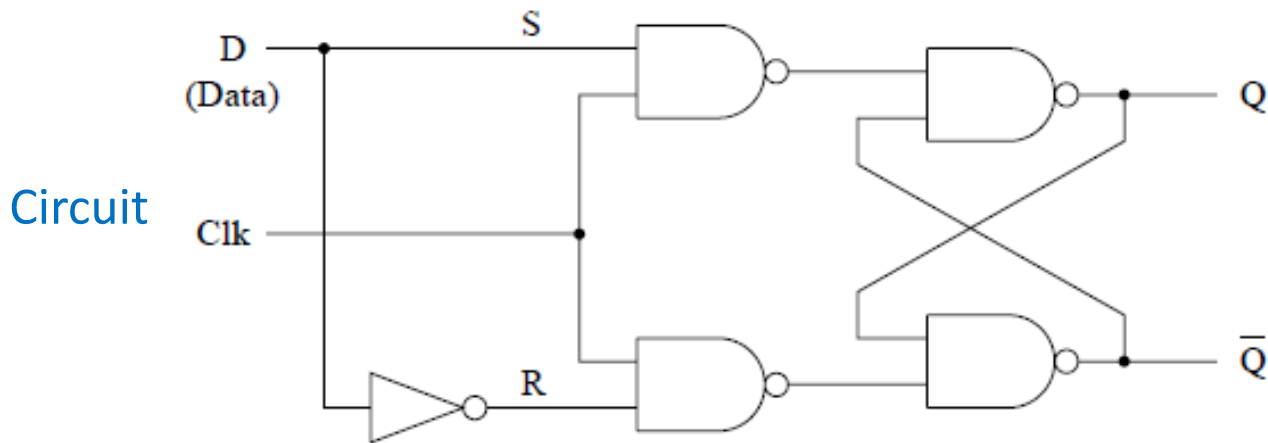


D latch is a special case of SR latch where S and R are derived from single input D

- When  $\text{clk} = 1$ 
  - the Q output is set to the value of D input
- When  $\text{clk} = 0$ 
  - the Q output retains its previous value irrespective of the D input


**D latch samples input data when clk is high and stores data until next clock pulse**
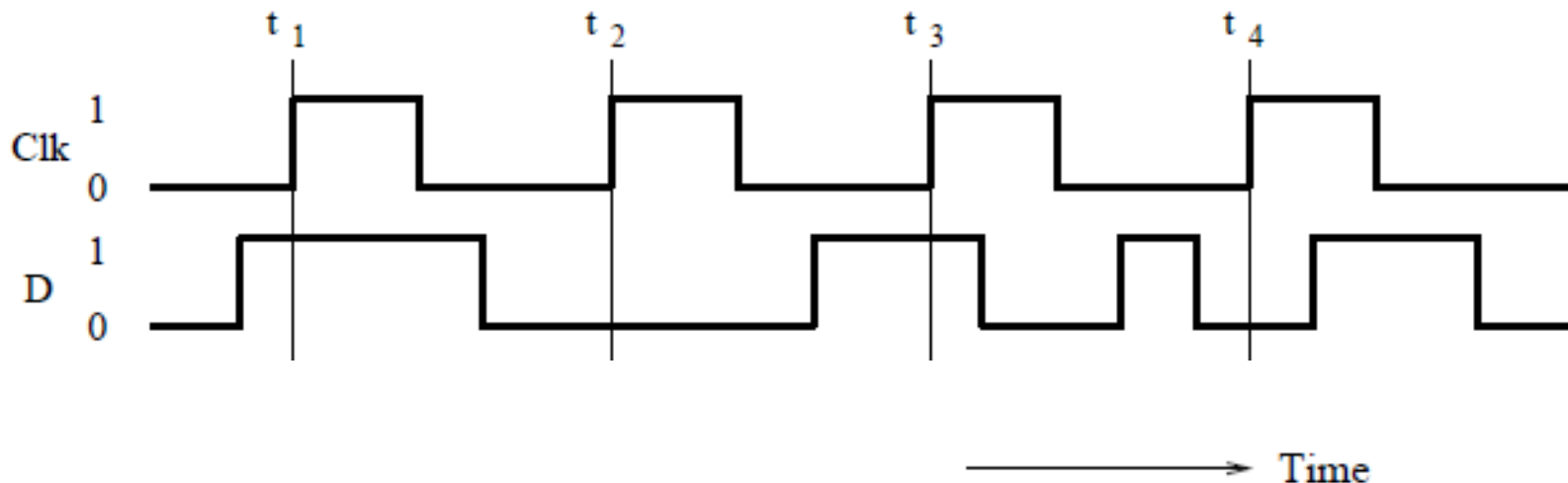
# Practice Exercise

The clock and D inputs for a gated D latch are shown below. Plot the Q output as a function of time.



# Practice Exercise: Solution


 


# Limitations of Latches


- Latches are sensitive only to clock levels (level-sensitive)
- When clock is high, latch output responds immediately to any changes in inputs
- Undesirable in circuits involving counters and shift registers
  - Immediate propagation of inputs to outputs may lead to incorrect operation
- **Solution: Master-slave flip flop**
  - Sensitive to clock signal transitions (edge-sensitive)
  - Outputs isolated from inputs at all times except at clock transitions
  - Positive edge triggering: data transfer occurs at 0->1 clock transition
  - Negative edge triggering: data transfer occurs at 1->0 clock transition

# Master-slave D flip-flop

Circuit

 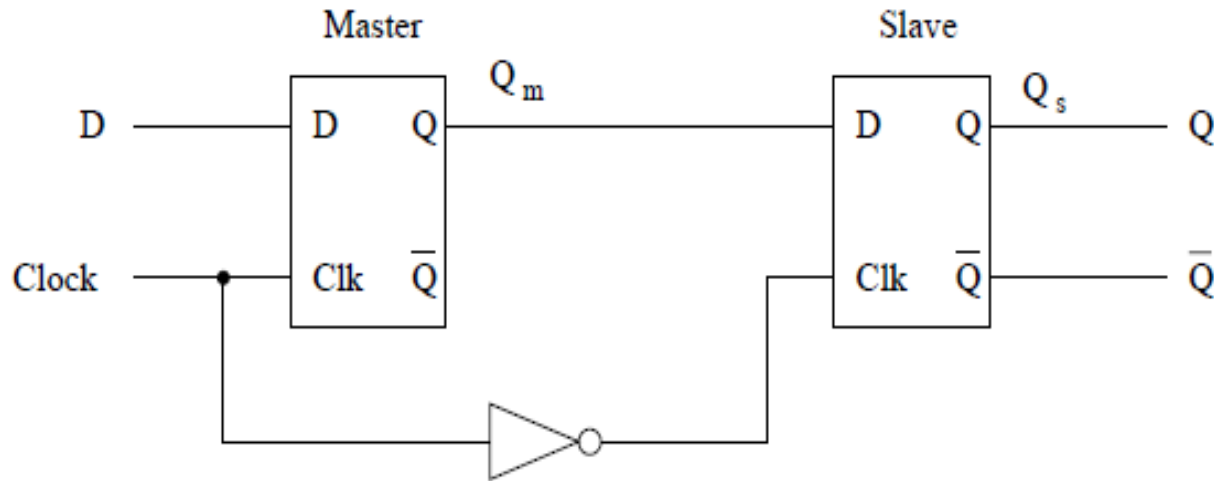


Example Timing Diagram

 

Graphical Symbol

# Master-slave D flip-flop

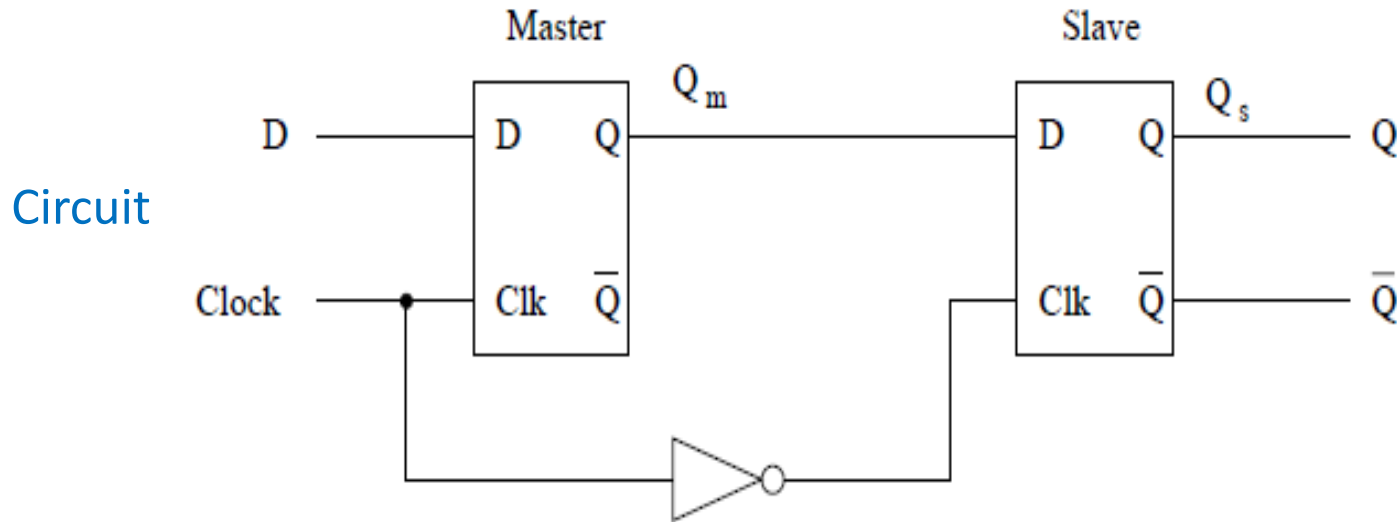


- Two gated D-latches (master and slave) together form a master-slave flip-flop
- When  $\text{clk} = 1$ :
  - D input is transferred to master's output, slave's output is unchanged
- When clock transitions from 1 to 0:
  - Master's contents ( $Q_m$ ) transferred to slave's output ( $Q$ ), master's output isolated from D-input
- D flip-flop is commonly used for temporary storage of data




# T flip-flop

Circuit

 

| T | $Q(t+1)$     |
|---|--------------|
| 0 | $Q(t)$       |
| 1 | $\bar{Q}(t)$ |


Truth Table

 


Graphical  
Symbol

# T flip-flop

Circuit

 


Example  
Timing  
Diagram

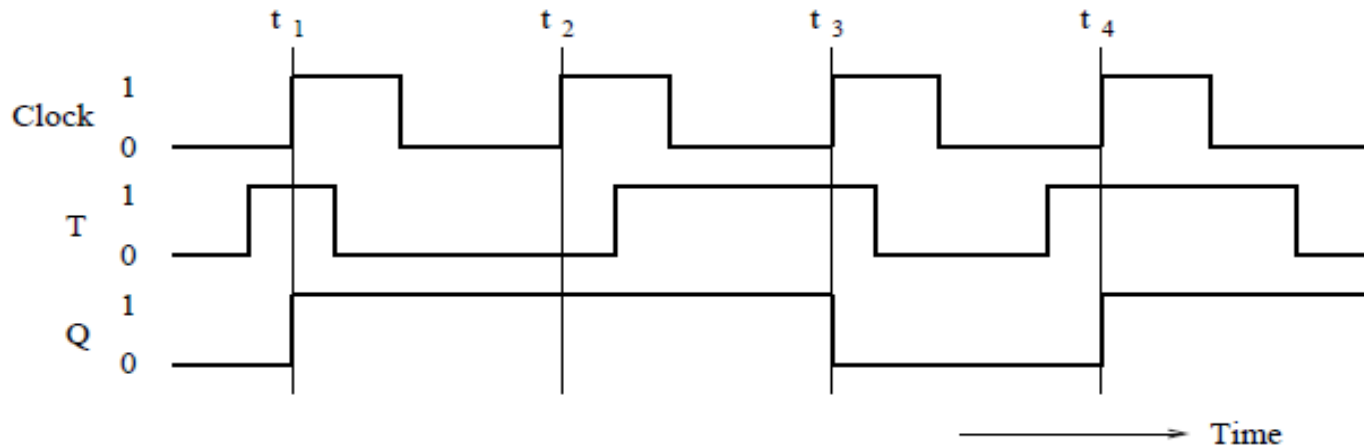

- T flip-flop toggles its state every cycle if its input T is equal to 1
- Useful in building counters


# JK flip-flop

Circuit

 

| J | K | $Q(t+1)$     |
|---|---|--------------|
| 0 | 0 | $Q(t)$       |
| 0 | 1 | 0            |
| 1 | 0 | 1            |
| 1 | 1 | $\bar{Q}(t)$ |


Truth Table

 

Graphical  
Symbol

# JK flip-flop

Circuit

 

- JK flip-flop combines the behavior of SR and T flip-flops
- When  $J = K = 1$ , it functions as a toggle (T flip-flop)
- For other input combinations, it acts as a SR flip-flop with  $J = S$  and  $K = R$
- JF flip-flop is versatile; can be used both for data storage and building counters