

ECE 341

Lecture # 5

Instructor: Zeshan Chishti
zeshan@ece.pdx.edu

October 13, 2014


Portland State University

Lecture Topics

- Computer Arithmetic
 - 2's Complement Representation
 - Addition and subtraction of signed integers
 - Binary Addition
 - Overflow Conditions
 - Ripple-carry Adders
 - Design of Fast Adders
 - Carry Lookahead Adders (CLA)
- Reference:
 - Chapter 9: Sections 9.1, 9.2

Two's Complement Representation

 - N-bit binary digit can represent any integer between -2^{N-1} and $+2^{N-1}-1$
- Most significant bit (MSB) indicates sign of the integer
- To obtain representation for a signed integer
 - Invert the bits (1's complement)
 - Add 1
 - E.g., $+4 = 0100$
 $-4 = 1011 + 1 = 1100$
- To add a +ve number, go clockwise,
- To add a -ve number, go anticlockwise



0 100 = + 4
1 100 = - 4

Addition and Subtraction – 2's Complement

Addition

- Bit pairs added from LSB to MSB
- Each addition takes bit values and *carry-in* as input, generates *sum* and *carry-out* as outputs
- *Carry-out* at any bit position becomes *carry-in* for next bit position

$$\begin{array}{r}
 \text{Carry-in } 0000 \leftarrow \text{ } \rightarrow 1100 \\
 \begin{array}{r}
 4 \quad 0100 \\
 + 3 \quad 0011 \\
 \hline
 7 \quad 0111
 \end{array}
 \qquad
 \begin{array}{r}
 -4 \quad 1100 \\
 + (-3) \quad 1101 \\
 \hline
 -7 \quad 11001
 \end{array}
 \end{array}$$

Sum $\swarrow \searrow$


Subtraction

- Take the 2's complement of the second operand
- Add to the first operand

$$\begin{array}{r}
 \begin{array}{r}
 4 \quad 0100 \\
 - (-3) \quad 1101 \\
 \hline
 \end{array}
 \Rightarrow
 \begin{array}{r}
 \text{Carry-in } 0000 \\
 4 \quad 0100 \\
 + 3 \quad +0011 \\
 \hline
 7 \quad 0111
 \end{array}
 \end{array}$$


Simpler addition/subtraction scheme makes two's complement the most common choice for integer number systems

Overflow in Integer Arithmetic

 

Adding two positive integers results in a negative integer

$5 + 3 = -8$
Should be +8

 

$-7 - 2 = +7$
Should be -9

Adding two negative integers results in a positive integer

When the result of an add/subtract cannot be represented by the same number of bits as the operands, overflow occurs

Overflow Conditions

$$\begin{array}{r} 5 \qquad 0111 \\ \underline{3 \quad 0011} \\ -8 \quad 1000 \\ \text{Overflow} \end{array}$$

$$\begin{array}{r} -7 \quad 1000 \\ \underline{-2 \quad 1100} \\ 7 \quad 10111 \\ \text{Overflow} \end{array}$$

For addition:

- Overflow cannot occur if the sign of two operands is different
- Overflow occurs when the sign of two operands is the same AND the sign of result is different from the sign of operands

For both addition and subtraction:

- Overflow occurs when the carry-in to MSB is different from the carry-out of MSB

Logic Specification for Binary Addition

| x_i | y_i | Carry-in c_i | Sum s_i | Carry-out c_{i+1} |
|-------|-------|----------------|-----------|---------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

At the i^{th} stage:

Input:

c_i is the carry-in

Output:

s_i is the sum


c_{i+1} carry-out to $(i+1)^{st}$ stage

$$s_i = \bar{x}_i \bar{y}_i c_i + \bar{x}_i y_i \bar{c}_i + x_i \bar{y}_i \bar{c}_i + x_i y_i c_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = y_i c_i + x_i c_i + x_i y_i$$

 
Example:

$$\begin{array}{r} X \\ + Y \\ \hline Z \end{array} = \begin{array}{r} 7 \\ + 6 \\ \hline 13 \end{array} = \begin{array}{r} 0 \ 1 \ 1 \ 1 \\ + 0 \ 0 \ 1 \ 1 \\ \hline 1 \ 1 \ 0 \ 1 \end{array}$$



Legend for stage i


Addition Logic for a Single Stage

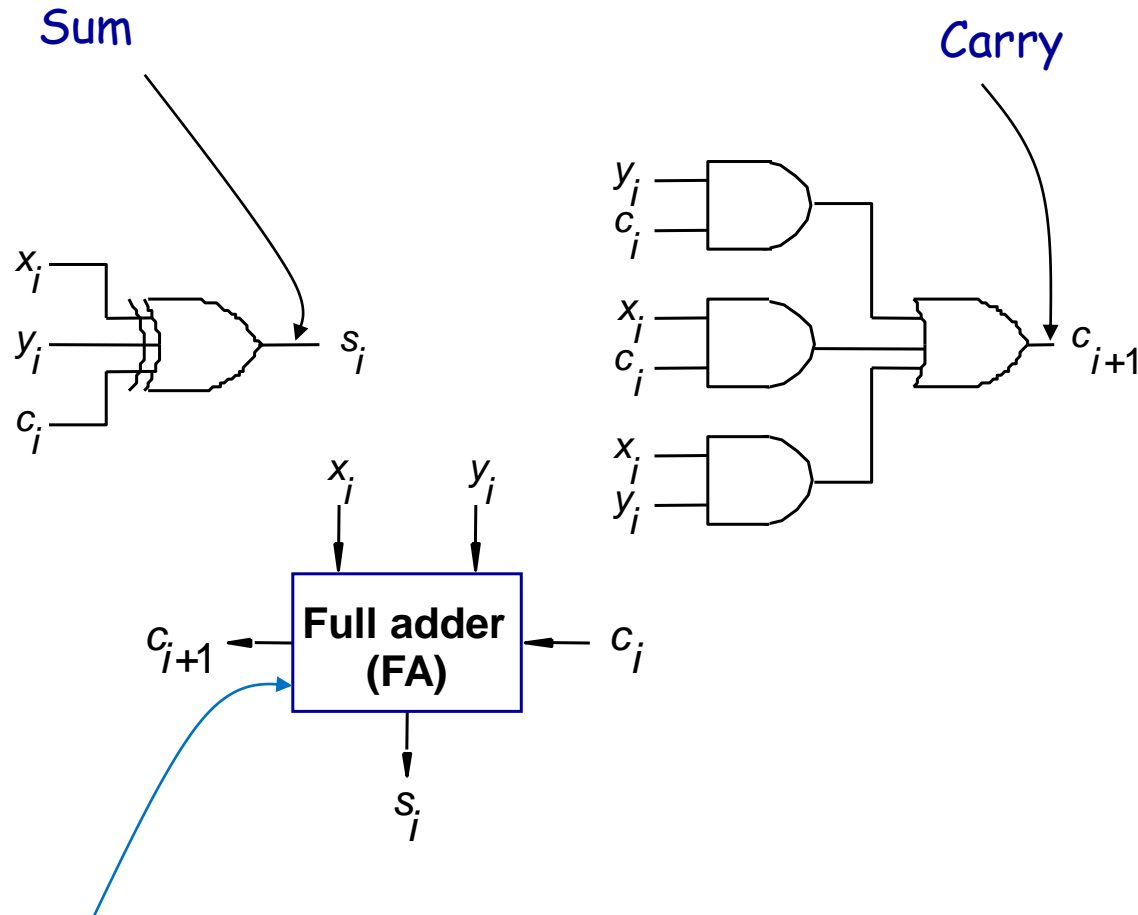

Full Adder (FA): Symbol for the complete circuit for a single stage of addition

n -bit Adder

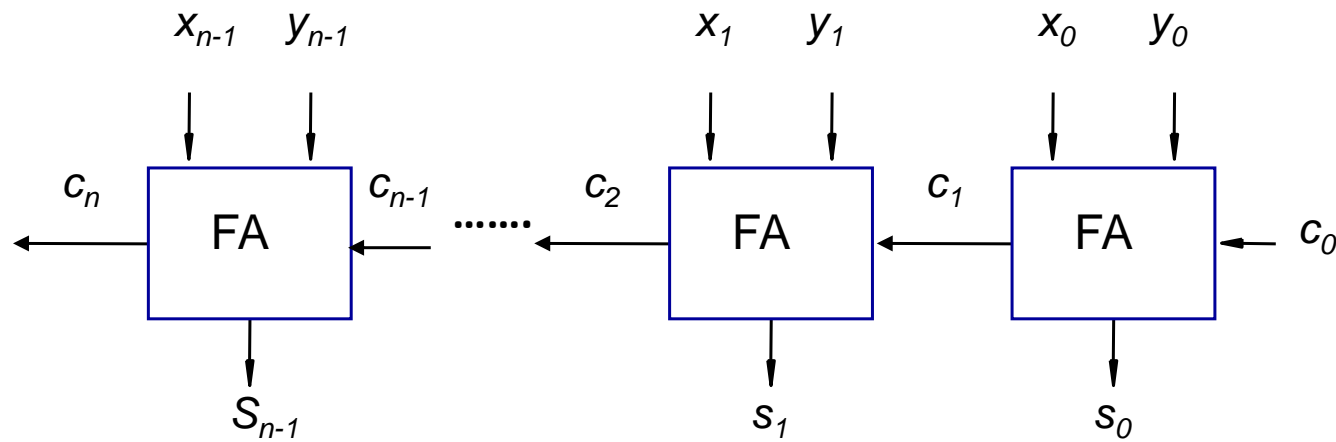- Cascade n full-adder (FA) blocks to form a n -bit adder.
- Carries propagate or ripple through this cascade, n -bit ripple carry adder




Most significant bit
(MSB) position

Least significant bit
(LSB) position

kn-bit Adder

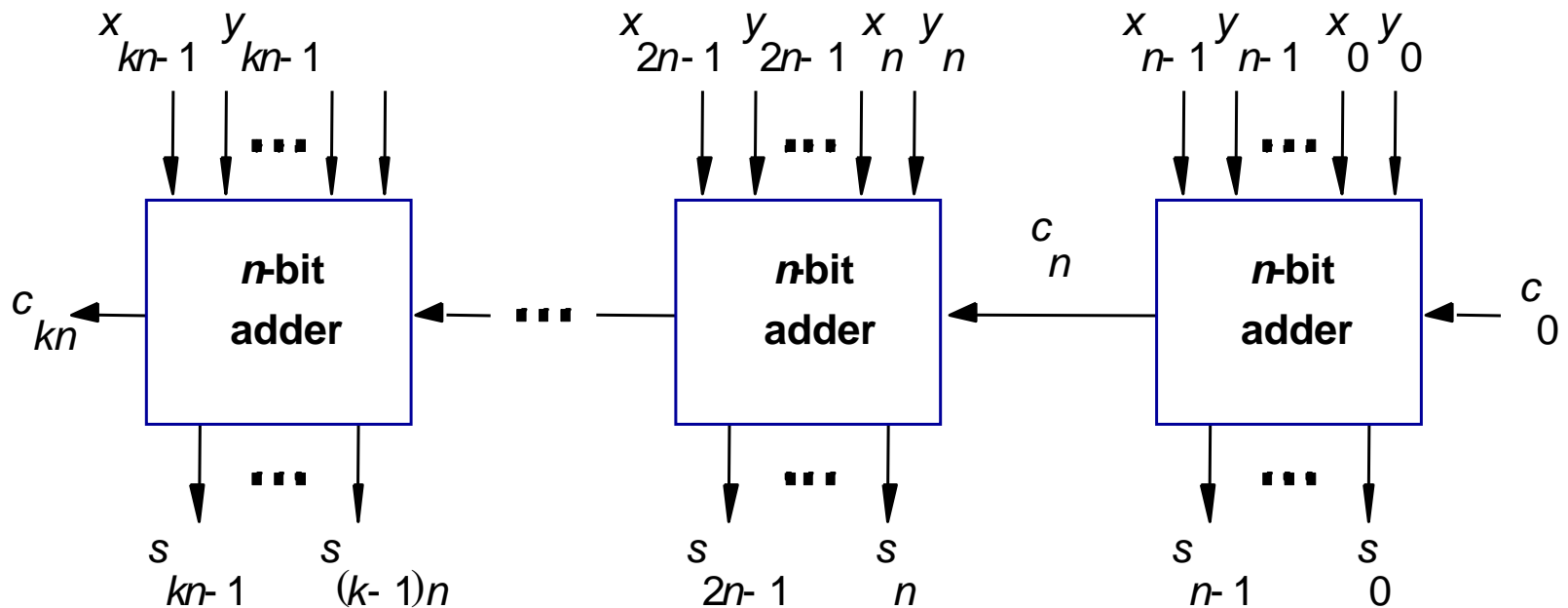Two numbers each having *kn*-bits can be added by cascading *k* *n*-bit adders
For example, 8 4-bit adders can be cascaded to add two 32-bit numbers




Each *n*-bit adder forms a block

Carries ripple or propagate through blocks, [Blocked Ripple Carry Adder](#)

n -bit Subtractor

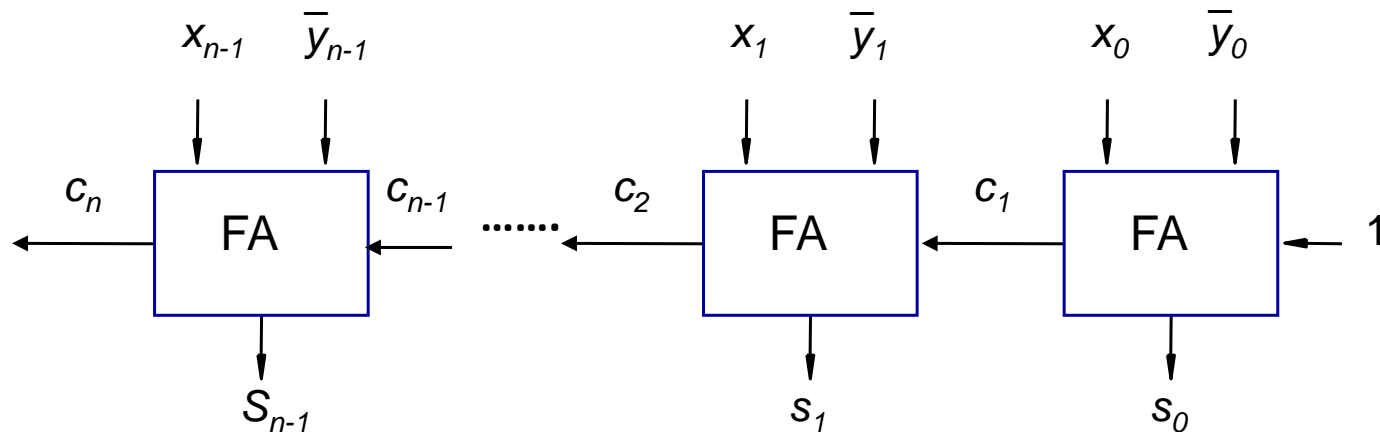
- Recall $X - Y$ is equivalent to adding 2's complement of Y to X .
- 2's complement is equivalent to 1's complement + 1.
- $X - Y = X + \bar{Y} + 1$
- Carry-in c_0 into the LSB position is equal to "1" to perform subtraction



Most significant bit
(MSB) position

Least significant bit
(LSB) position

n -bit Adder/Subtractor

 

Add/sub control = 0 implies addition.

Add/sub control = 1 implies subtraction.

Detecting Overflows

Recall that for **addition**

- Overflow can occur only when the sign of two operands is the same
- Overflow occurs if the sign of result is different from the sign of operands
- Recall that the MSB represents the sign.
 - $x_{n-1}, y_{n-1}, s_{n-1}$ represent the sign of operand x , operand y and result s respectively
- Circuit to detect overflow in an **n-bit adder** can be implemented as:


$$Overflow = x_{n-1}y_{n-1}\bar{s}_{n-1} + \bar{x}_{n-1}\bar{y}_{n-1}s_{n-1}$$

Recall that for both **addition/subtraction**,

- Overflow occurs when carry-in to MSB is different from carry-out of MSB
- Simpler circuit to detect overflow in an **n-bit adder/subtractor** is:

$$Overflow = c_n \oplus c_{n-1}$$


Computing the Add Time

 

Consider 0^{th} stage:


- c_1 is available after 2 gate delays.
- s_0 is available after 1 gate delay.

 - c_i needed to compute s_i
- Carry propagation is the critical path in a ripple-carry adder



Computing the Add Time (contd..)

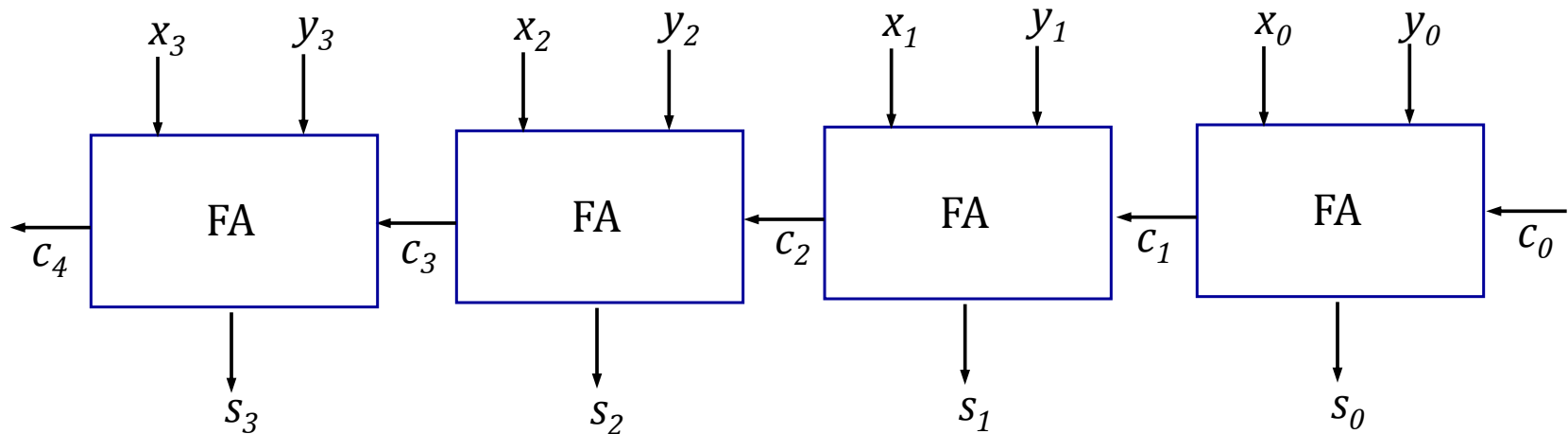Cascade of 4 Full Adders, or a 4-bit adder



- s_0 available after 1 gate delays, c_1 available after 2 gate delays.
- s_1 available after 3 gate delays, c_2 available after 4 gate delays.
- s_2 available after 5 gate delays, c_3 available after 6 gate delays.
- s_3 available after 7 gate delays, c_4 available after 8 gate delays.

**For an n -bit ripple adder, s_{n-1} is available after $2n-1$ gate delays
 c_n is available after $2n$ gate delays.**

Fast Addition

Recall the equations:

$$s_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Second equation can be written as:

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

We can write:

$$c_{i+1} = G_i + P_i c_i$$

$$\text{where } G_i = x_i y_i \text{ and } P_i = x_i + y_i$$

- G_i is called **generate** function and P_i is called **propagate** function
- G_i and P_i computed *only* from x_i and y_i and *not* c_i , thus they can be computed in **one** gate delay after X and Y are applied to the inputs of an n -bit adder

Carry Lookahead Adder (CLA)

$$c_{i+1} = G_i + P_i c_i$$

$$c_i = G_{i-1} + P_{i-1} c_{i-1}$$

$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} c_{i-1})$$

continuing

$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} c_{i-2}))$$

until

$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0$$

- c_{i+1} in the above equation depends only on propagate functions, generate functions and c_0
- Calculation of c_{i+1} no longer requires calculation of c_i , c_{i-1} , c_{i-2} etc.
 \Rightarrow all carries can be computed in parallel
- This is called **carry lookahead addition (CLA)**

Understanding Carry-Lookahead Addition

- CLA relies on **generate (G)** and **propagate (P)** functions
- An n -bit CLA computes G_i and P_i at each of its n stages

$$G_i = x_i y_i \text{ and } P_i = x_i + y_i$$

- $G_i = 1$ implies that stage i **generates** a carry-out of 1, independent of its carry-in
- $P_i = 1$ implies that stage i **propagates** a carry-in of 1 from its input to its output
- The carry-out c_{i+1} of stage i is equal to 1, if:
 - Stage i generates a carry-out (i.e., $G_i = 1$), or
 - Any stage j , such that $j < i$, generates a carry-out (i.e., $G_j = 1$) and all the stages between j and i , including i , propagate the carry (i.e., $P_{j+1} = P_{j+2} = \dots = P_i = 1$), or
 - $c_0 = 1$ and all the stages up to and including stage i propagate the carry (i.e., $c_0 = P_0 = P_1 = \dots = P_i = 1$)
- Therefore, the general expression for c_{i+1} in a CLA is:

$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0$$

CLA Example

- The general expression for c_{i+1} in CLA is:

$$\text{➤ } c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0$$

- Consider 4-bit addition. The carries can be implemented as:

$$\text{➤ } c_1 = G_0 + P_0 c_0$$


$$\text{➤ } c_2 = G_1 + P_1 G_0 + P_1 P_0 c_0$$

$$\text{➤ } c_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$


$$\text{➤ } c_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$

- Above equations can be used to implement a 4-bit carry-lookahead adder

4-bit Carry Lookahead adder

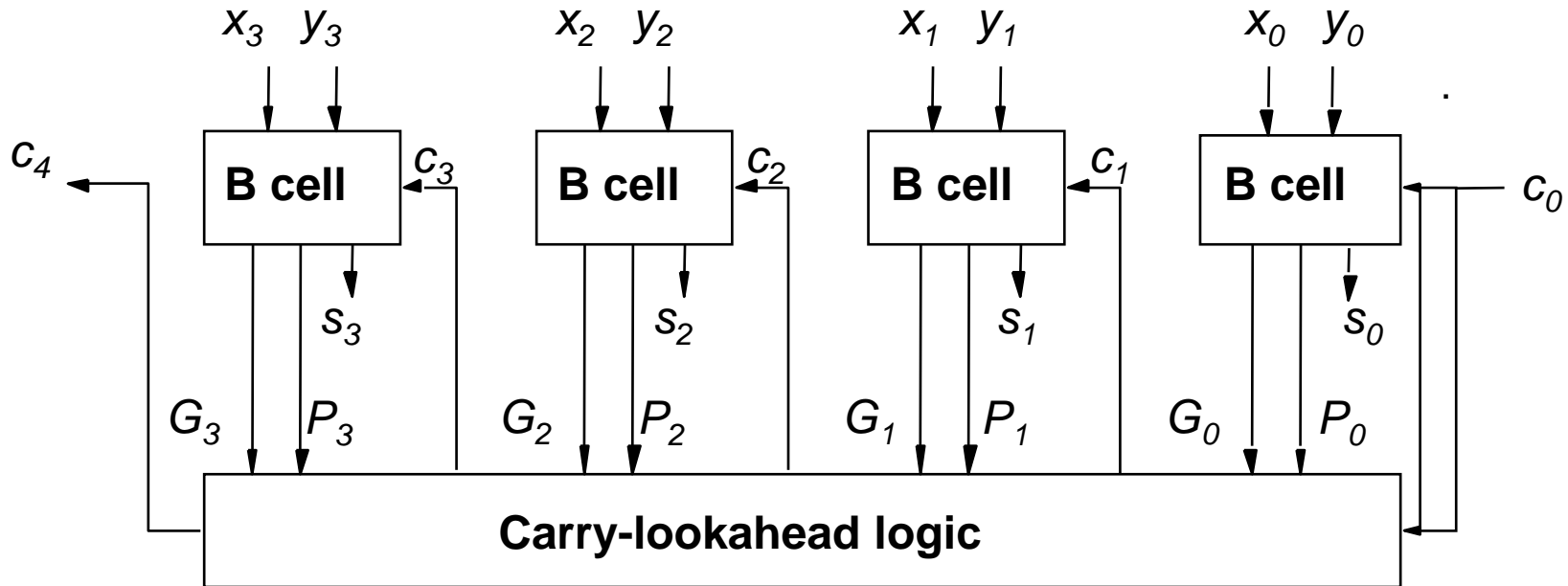

B-cell for a single stage

 

P_i implemented as XOR of x_i and y_i instead of $x_i + y_i$. This is ok because when $x_i = 1, y_i = 1, G_i$ is equal to 1.